

✓ Fall time ✓

→ To calculate fall time (t_f), assume that V_{in} changes from 0 to V_{DD} at time $t=0$

The initial condition at the output is $V_{out}(0) = V_{DD}$. When the input is switched, the nFET goes active while the pFET is driven into cutoff. In terms of the switch models, the nFET switch is closed and pFET switch is open.

This gives the simplified discharge circuit shown in fig (a). The capacitor C_{out} is initially charged to a voltage V_{DD} and is allowed to discharge to 0V through the nFET resistance R_n . The discharging current is given by.

$$i = -C_{out} \frac{dV_{out}}{dt} = \frac{V_{out}}{R_n}$$


(Differential eqn for the discharge current)


Solving with the initial condition $V_{out}(0) = V_{DD}$ results in the form

$$V_{out}(t) = V_{DD} e^{-t/\tau_n} \rightarrow (2)$$

where $\tau_n = R_n C_{out} \rightarrow (3)$ is the nFET time constant

The function is plotted in fig (b).

 

 

The fall time t_f may be defined as -
 it is the time interval from $V_1 = 0.9V_{DD}$ to $V_0 = 0.1V_{DD}$, which are respectively known as the 90% and the 10% voltages as referenced to the full rail swing of V_{DD} .

Take a natural logarithm to the eq (2) and rearrange.

$$\ln V_{out}(t) = \ln V_{DD} (-t/\tau_n)$$

$$-t/\tau_n = \ln V_{out}(t) - \ln V_{DD}$$

$$t = \tau_n [\ln V_{DD} - \ln V_{out}(t)]$$

$$t = \tau_n \ln \left[\frac{V_{DD}}{V_{out}} \right] \rightarrow (4)$$

$$\left[\ln(a) - \ln(b) = \ln(a/b) \right]$$

$$\text{fall time } t_f = t_y - t_x$$

$$= \tau_n \ln \left(\frac{V_{DD}}{0.1V_{DD}} \right)$$

$$= \tau_n \ln \left(\frac{1}{0.1} \right) = \tau_n \ln \left(\frac{1}{0.9} \right)$$

$$= T_0 \ln(9)$$


$$= 2.2 T_0$$

$$t_f = 2.2 T_0$$

The output fall time in a generic digital logic gate is usually called the output high-to-low time t_{HL} .

$$t_{HL} = t_f$$

The rise time t_r

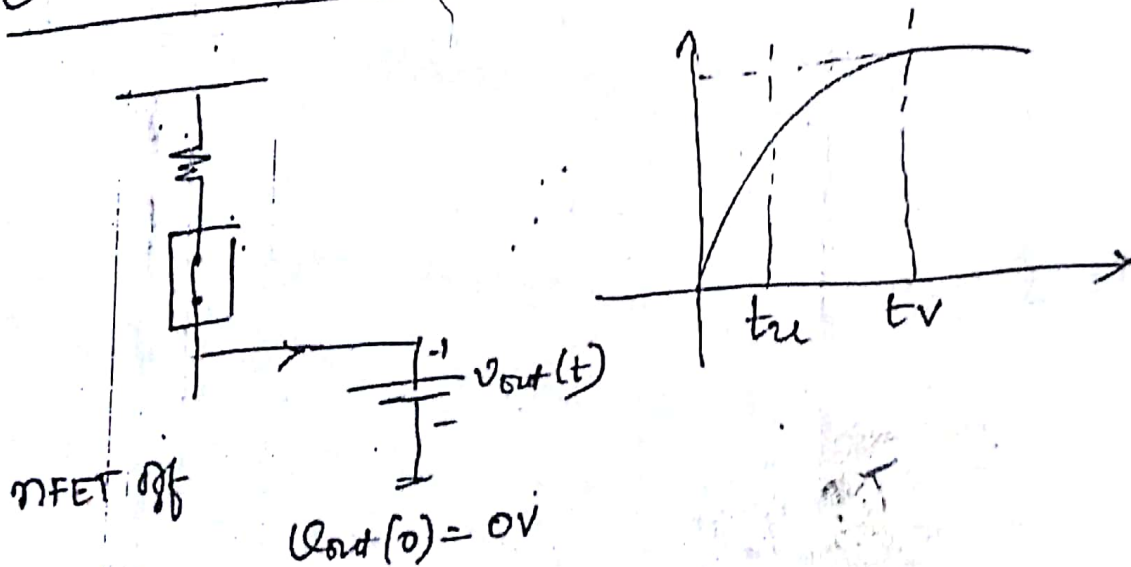

To calculate rise time t_r
Initially input voltage is at $V_{in} = V_{DD}$ and
i.e. switched to $V_{in} = 0V$ at $t=0$
this turns on the pFET while simultaneously
driving the nFET into cutoff, this gives the
simplified charging circuit shown in the fig (2)

The output voltage at $t=0$ is given by.

$$V_{out}(0) = 0V.$$

The charging current is given by.

$$I = C_{out} \frac{dV_{out}}{dt} = \frac{V_{DD} - V_{out}}{R_p} \rightarrow (1)$$

$$V_{out}(t) = V_{DD} \left(1 - e^{-t/\tau_p}\right) \rightarrow (2)$$

τ_p is the time constant of PFET and is given by.

$$\tau_p = R_p C_{out} \rightarrow (3)$$

Shows the v_{out} voltage as a function of time. The rise time i.e. taken between 10% and 90% points such that.

$$t_r = t_v - t_u$$

Taking natural logarithm, & rearrange the terms in eq (2).

$$t = \tau_p \ln \left(\frac{V_{DD}}{V_{out}} \right)$$

* from eq (2).

$$(1 - e^{-t/\tau_p}) = \frac{V_{out}}{V_{DD}}$$

$$-e^{-t/\tau_p} = \frac{V_{out}}{V_{DD}} - 1$$

$$t/\tau_p = \ln\left(\frac{V_{out}}{V_{DD}}\right) - \ln(1)$$

$$t = \tau_p \ln\left(\frac{V_{out}}{V_{DD}}\right) - \tau_p \ln(1)$$

~~$$t = \tau_p \ln\left(\frac{V_{DD}}{V_{out}}\right)$$~~

$$t_x = \tau_p \ln\left(\frac{V_{out}}{V_{DD}}\right)$$

$$= \tau_p \ln\left(\frac{0.9V_{DD}}{V_{DD}}\right) - \tau_p \ln\left(\frac{0.1V_{DD}}{V_{DD}}\right)$$

$$= \tau_p \ln\left(\frac{0.9}{0.1}\right) = \tau_p \ln 9$$

$$t_x = \ln(9) \tau_p = 2.2 \tau_p$$

$$t_r = t_{LH}$$