

Block diagram of power electronic system :-

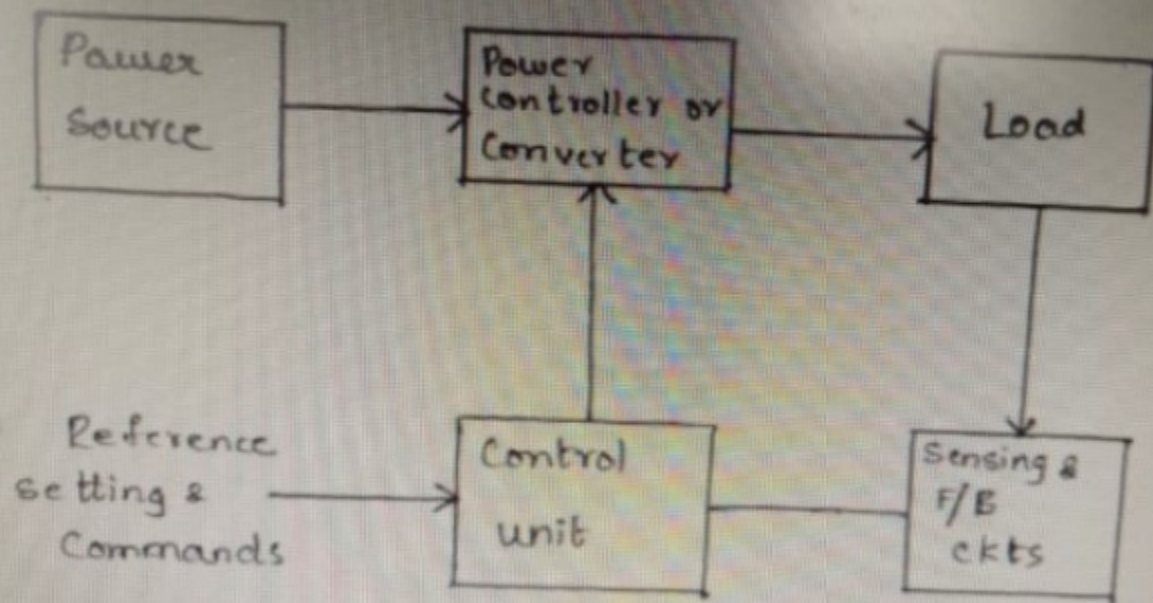


Figure shows the block diagram of the power system using a power converter or controller.