

Dayananda Sagar College of Engineering
Department of Electronics and
Communication

FUNDAMENTALS OF VLSI DESIGN

By
Dr.Usha. C

MODULE-3

CMOS Sub System Design

Introduction

Most Chip functions can be divided into the following categories:

1. Datapath operators
 2. Memory elements
 3. Control structures
 4. Special-purpose cells
 - I/O
 - Power distribution
 - Clock Generation and distribution
 - Analog
- CMOS system design consists of partitioning the system into subsystems
 - Many options exist that makes tradeoffs between
 - Speed
 - Density
 - Programmability
 - Ease if design
 - Other variables

Datapath Operators

- Benefit from the structured design principles of hierarchy, regularity, modularity and locality
- N identical circuits used to process N-bit data
- Related data operators are placed physically adjacent to each other to reduce wire length and delay
- Data is arranged to flow in one direction, while control signals are introduced in a direction orthogonal to the dataflow
- Common datapath operators include
 - Adders
 - One/Zero detectors
 - Comparators
 - Counters
 - Boolean logic Units
 - Error correcting code blocks
 - Shifters
 - Multipliers
 - Dividers

Addition/Subtraction



- Addition forms basis for many processing operations from counting to multiplication to filtering
- Adder architectures serve different speed/ area requirements

Single Bit Addition

Half Adder

Full Adder

Full Adder Design(CMOS Circuit)

  



A Compact design to reduce the number of transistor is that S can be factored to reverse Cout term

PTL/CPL logic for Full adder Design


Transmission Gate Full Adder Design

Table 8.2		Truth table for full adder					
<i>A</i>	<i>B</i>	<i>C</i>	<i>G</i>	<i>P</i>	<i>K</i>	<i>C_{out}</i>	<i>S</i>
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

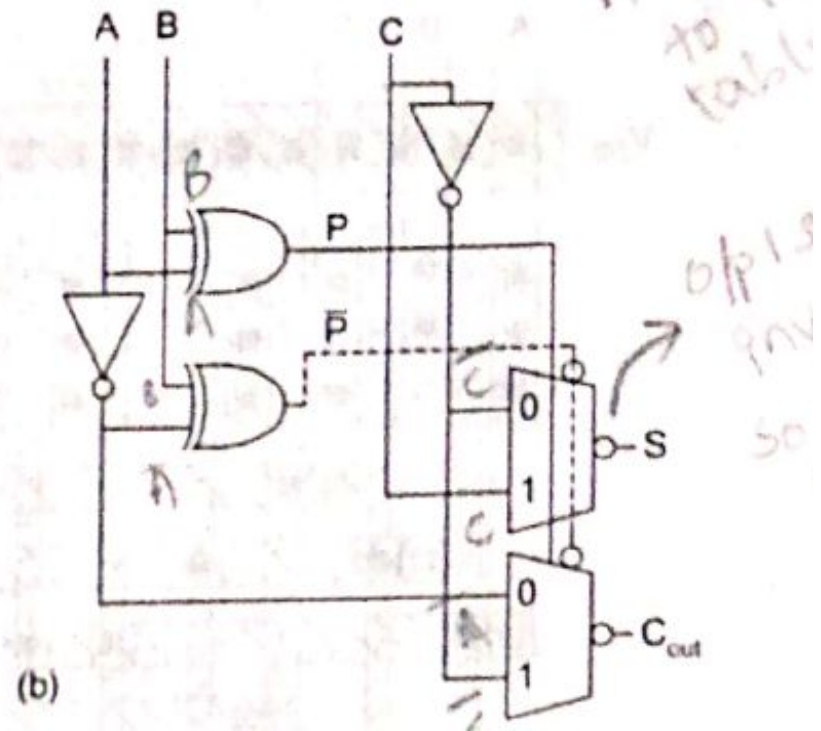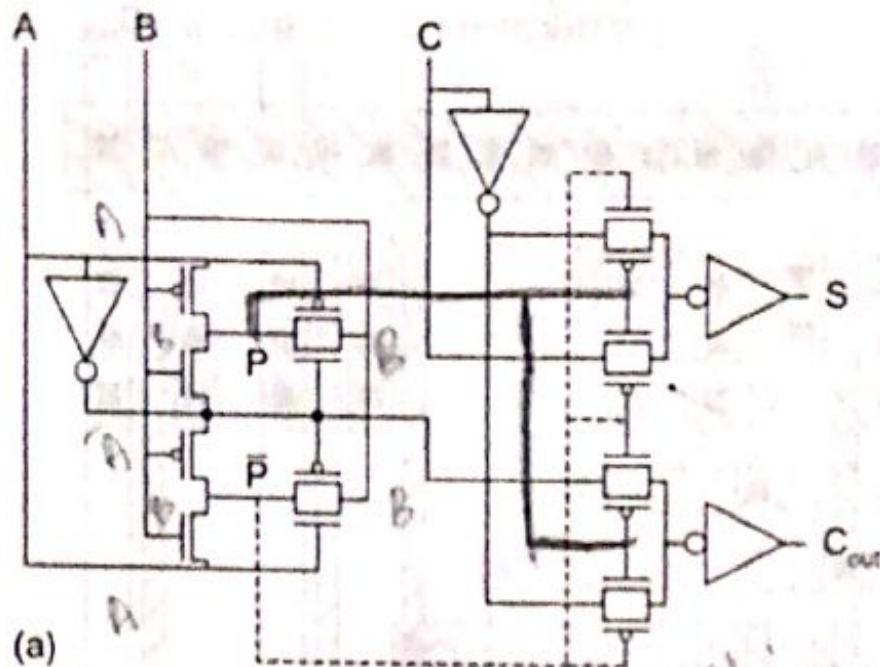
Full adder Design using Transmission gates to form Multiplexers and XOR's



Zuhang Full Adder

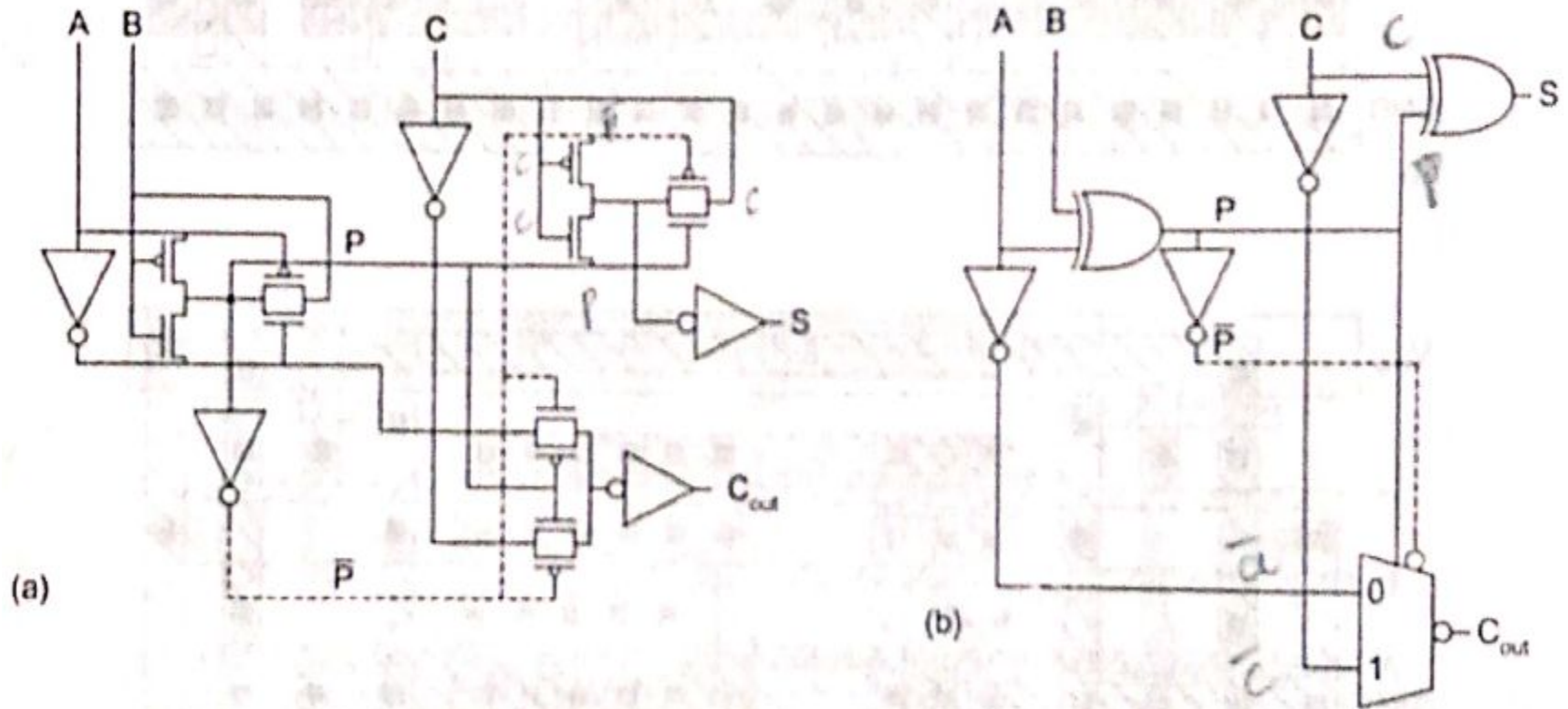



Dual Rail Domino Full Adder

 

Carry Propagate Addition


BN.....B
AN.....A1

  - N-bit adder called CPA
 - Each sum bit depends on all previous carries
 - How do we compute all these carries quickly?




Carry Ripple Adder

 - Simplest design: cascade full adders
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry (small delay for carry signal)



 - Critical path passes through majority gate
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



Carry Generation and Propagation

For a full adder, define what happens to carries


- **Generate:** $C_{out} = 1$, independent of C
 - $G = A \cdot B$
- **Propagate:** $C_{out} = C$
 - $P = A \oplus B$
- **Kill:** $C_{out} = 0$, independent of C
 - $K = \overline{A} \cdot \overline{B}$


Generate and Propagate for groups spanning $i:j$

- $G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$
- $P_{i:j} = P_{i:k} \cdot P_{k-1:j}$



 - Base Case
 - $G_{i:i} \equiv G_i = A_i \cdot B_i, \quad G_{0:0} = G_0 = C_{in}$
 - $P_{i:i} \equiv P_i = A_i \oplus B_i, \quad P_{0:0} = P_0 = 0$
- Sum: $S_i = P_i \oplus G_{i-1:0}$



 

shared bitwise
propagate-generate
(PG) logic

$$G_{i:j} = G_{i:k} + P_{i:k} \square G_{k-1:j} \qquad P_{i:j} = P_{i:k} \square P_{k-1:j}$$

Combines pair of smaller groups is called valency-2
group PG logic.

To use fewer stages for carry propagation, higher valency
comprising more complex gates is possible, e.g. valency-4:

$$P_{i:j} = P_{i:k} \square P_{k-1:l} \square P_{l-1:m} \square P_{m-1:j} \qquad i \geq k > l > m > j$$

$$G_{i:j} = G_{i:k} + P_{i:k} \left(G_{k-1:l} + P_{k-1:l} \left(G_{l-1:m} + P_{l-1:m} \square G_{m-1:j} \right) \right)$$

Higher Valency Groups

□ Valency-2

- Propagate
- Generate

$$P_{i,j} = P_{i,k} P_{k-1,j}$$

$$G_{i,j} = G_{i,k} + P_{i,k} G_{k-1,j}$$

□ Valency-3

- Propagate
- Generate

$$P_{i,j} = P_{i,k} P_{k-1,l} P_{l-1,j}$$

$$G_{i,j} = G_{i,k} + P_{i,k} (G_{k-1,j} + P_{k-1,l} G_{l-1,j})$$

□ Valency-4


- Propagate
- Generate

$$P_{i,j} = P_{i,k} P_{k-1,l} P_{l-1,m} P_{m-1,j}$$

$$G_{i,j} = G_{i,k} + P_{i,k} (G_{k-1,j} + P_{k-1,l} (G_{l-1,m} + P_{l-1,m} G_{m-1,j}))$$

PG Carry-Ripple Addition
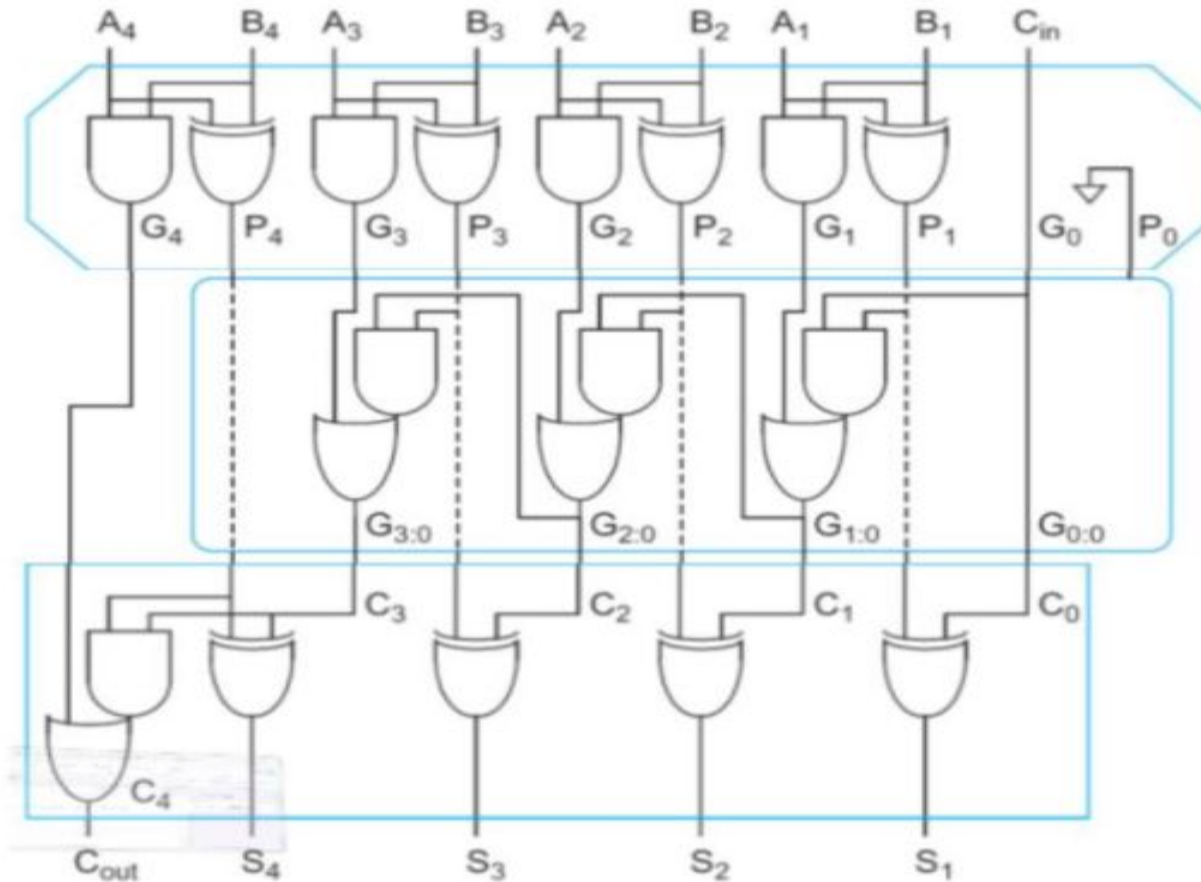
$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = A_i B_i + (A_i \oplus B_i) C_{i-1} = G_i + P_i C_{i-1}$$




$$C_i = G_i + P_i C_{i-1}$$


Black Cell: Group Generate and propagate logic

Gray Cell: Group generate logic





Black cell

 


Gray cell

 

Buffer

   
 


Adder architecture diagram

 


$$C_{out} = G_{N:0} = G_N + P_N G_{N-1:0}$$

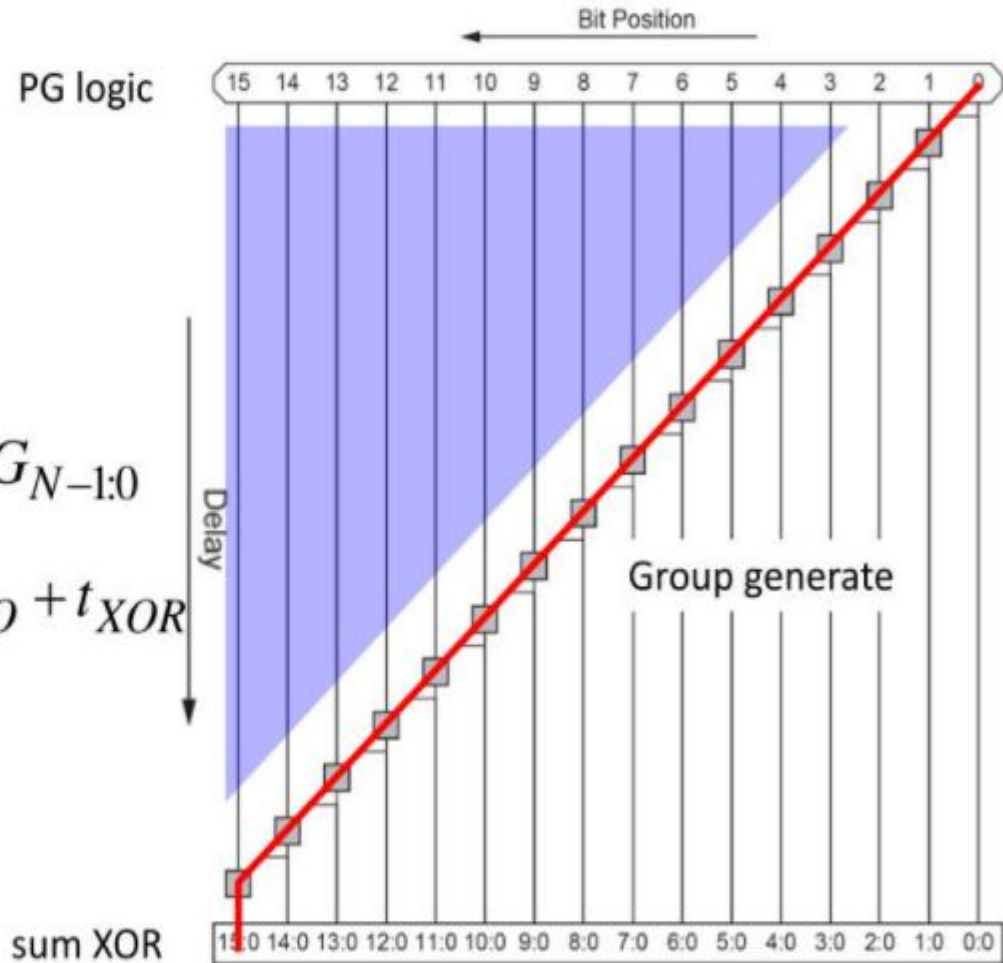
 
$$t_{ripple} = t_{pg} + (N-1)t_{AO} + t_{XOR}$$



 PG network to remove extraneous inverters





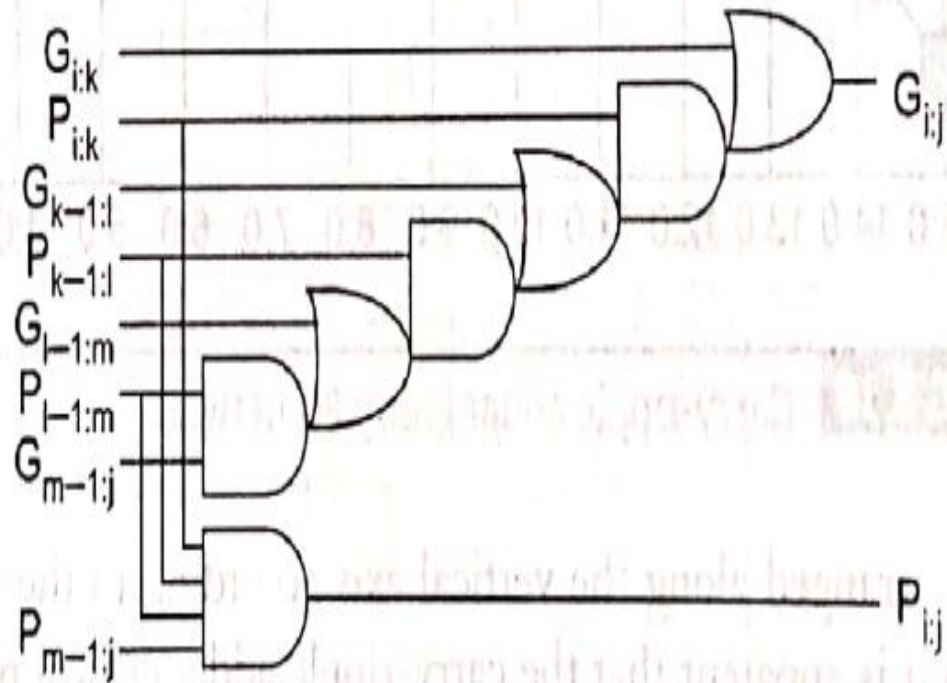 Reduce the number of stages by using higher valency cells





Manchester Carry Chain Adder


Carry Chain Designs

 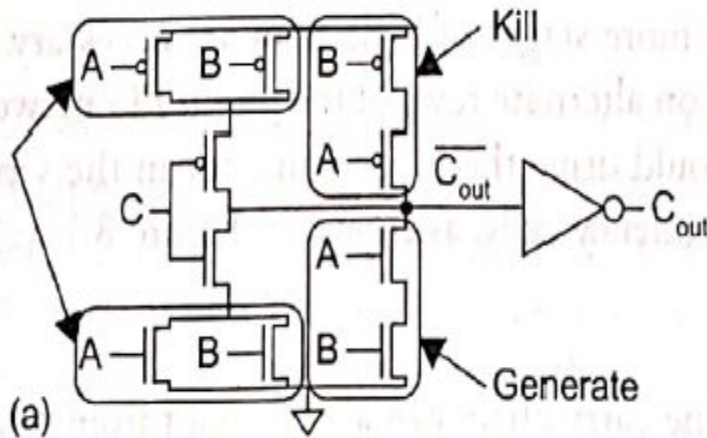

Multiple stages

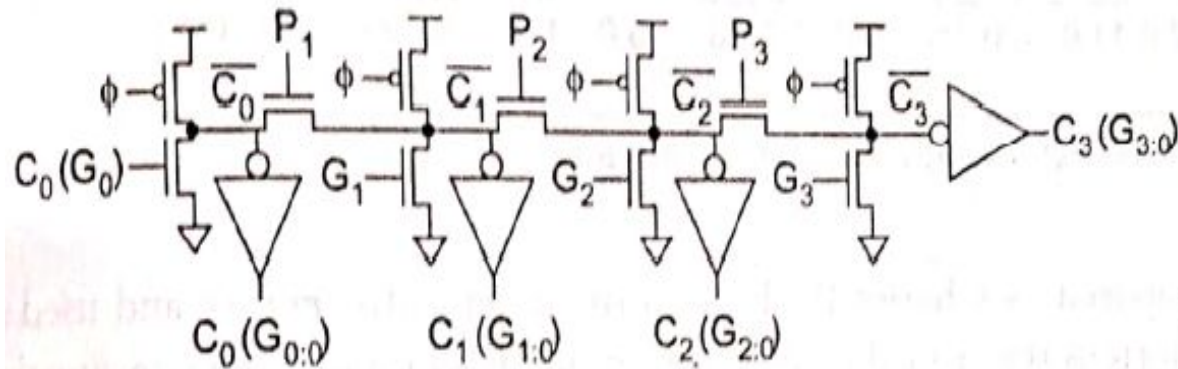 

(b)

 


(c)

$$C_0 = G_{0:0} = C_0$$


$$C_1 = G_{1:0} = G_1 + P_1 C_0$$

$$C_2 = G_{2:0} = G_2 + P_2 (G_1 + P_1 C_0)$$
 
$$C_3 = G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 C_0))$$




 Equivalence of Manchester Carry Chain and Multiple output domino gate




Manchester Carry Chain Adder group PG network

Carry Skip Adder

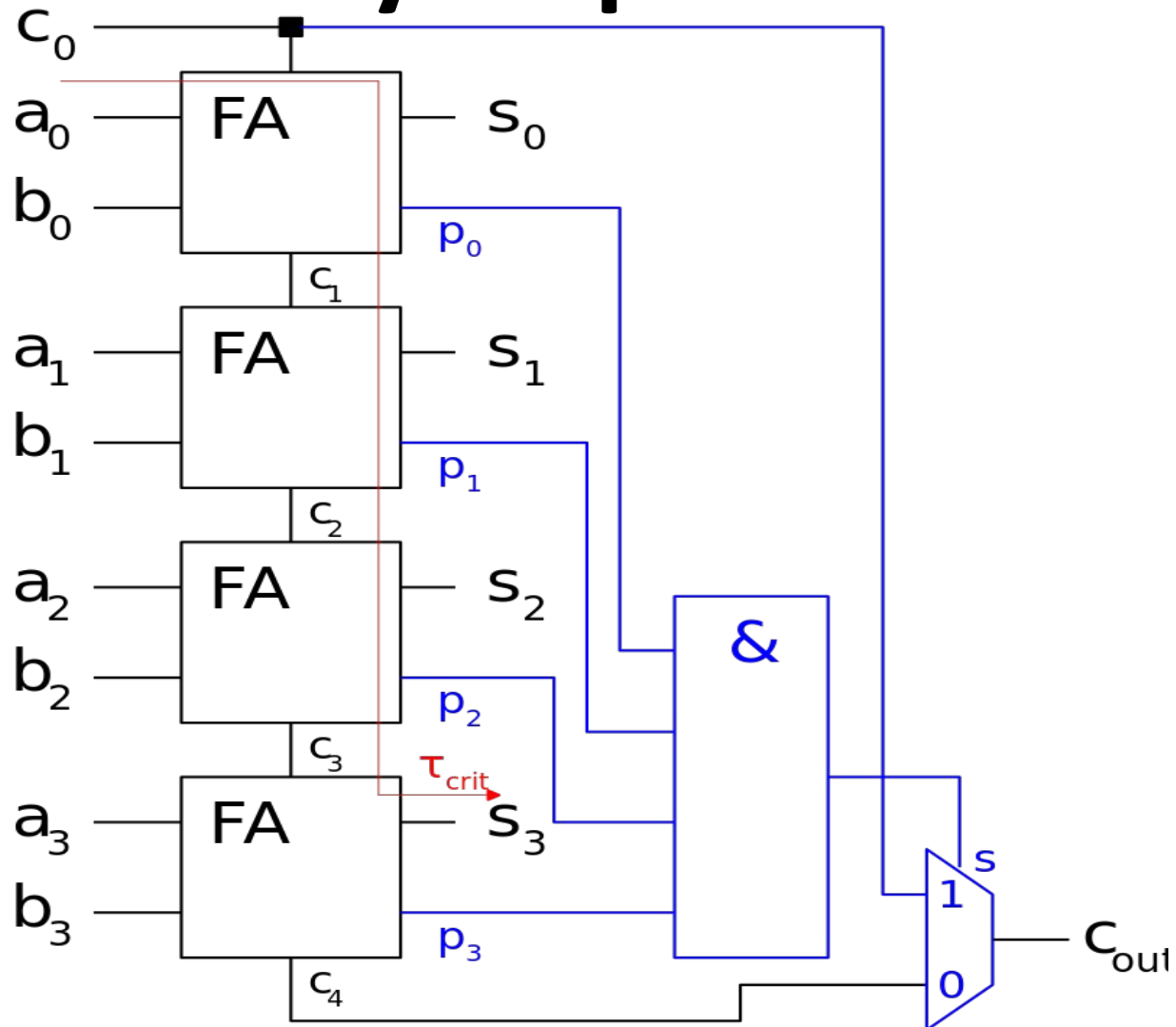

4-bit Block Carry-Skip Adder

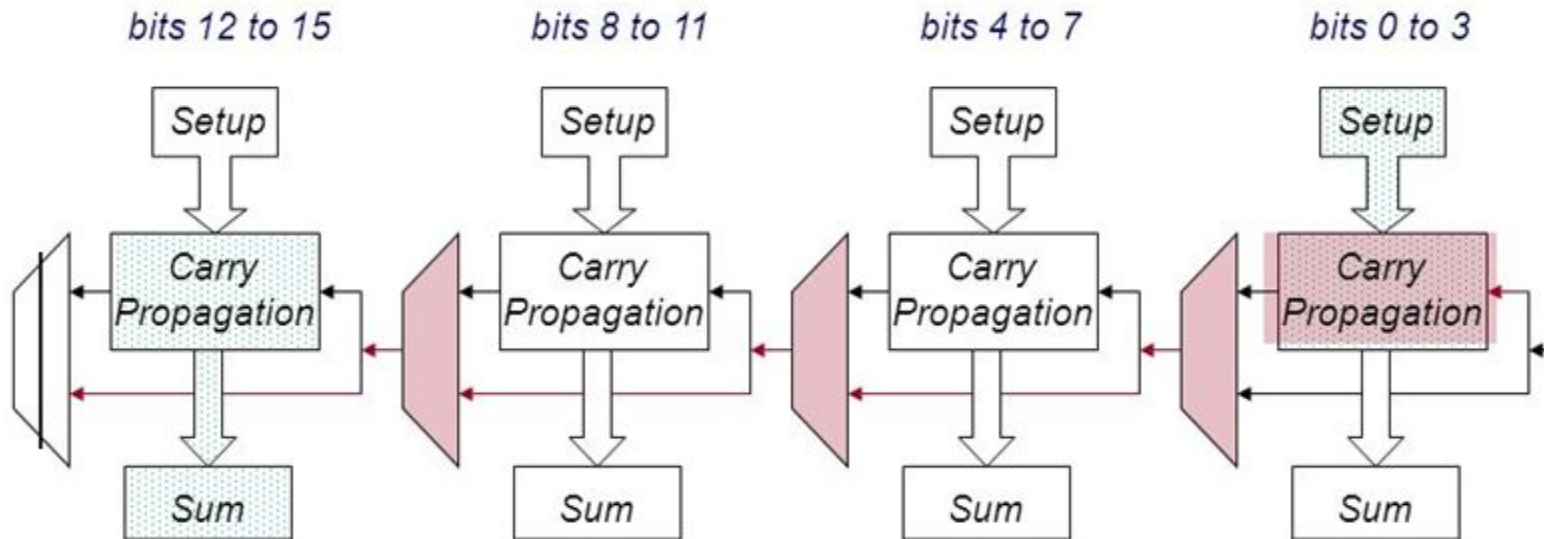


Worst-case delay → carry from bit 0 to bit 15 = carry generated in bit 0, *ripples* through bits 1, 2, and 3, *skips* the middle two groups (B is the group size in bits), *ripples* in the last group from bit 12 to bit 15

$$T_{add} = t_{setup} + B t_{carry} + ((N/B) - 1) t_{skip} + (B - 1) t_{carry} + t_{sum}$$

For k n -bit groups ($N = nk$)

$$t_{skip} = t_{pg} + [2(n - 1) + (k - 1)] t_{AO} + t_{xor}$$

- Carry-ripple is slow through all N stages
- Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal

 



 


FIGURE 11.18 Carry-skip adder PG network

Variable Group Size Carry Skip Adder

 


Carry Skip adder Manchester Stage

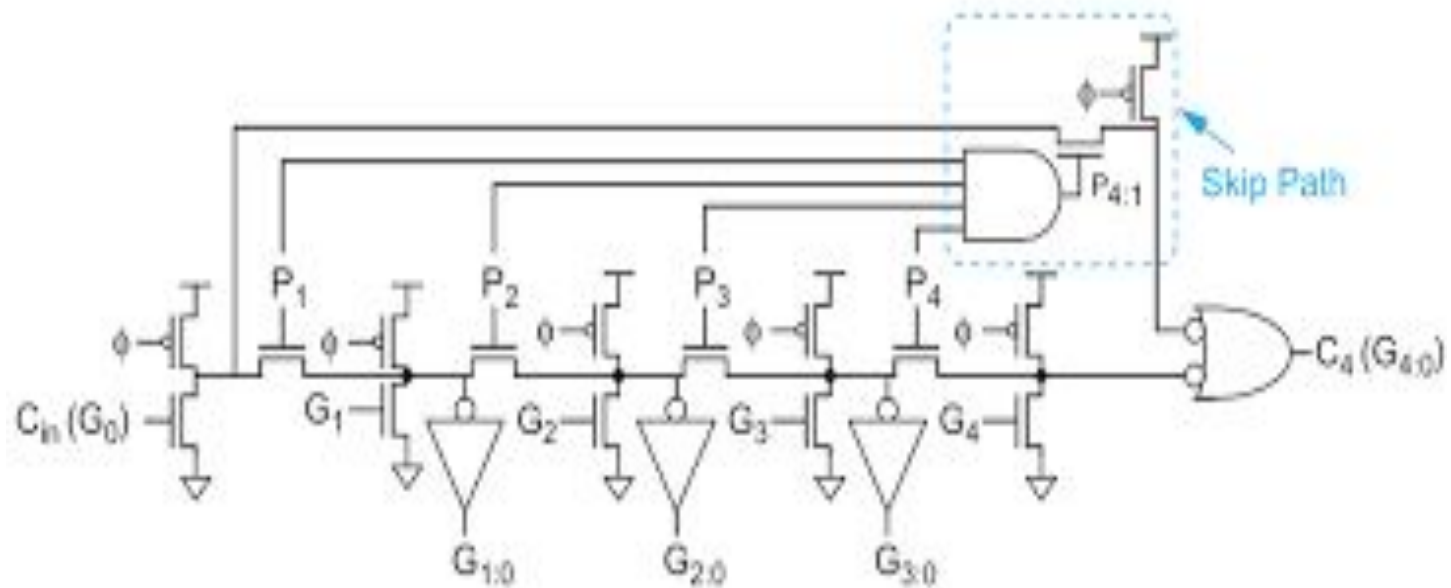

Carry Lookahead Adder

 - Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel
- Uses higher-valency cells with more than two inputs



$$t_{cla} = t_{pg} + t_{pg(n)} + \left[(n-1) + (k-1) \right] t_{AO} + t_{xor}$$

CLA PG Network



 


FIG 10.27 Carry-lookahead adder group PG network

Improved CLA PG Network

 


Higher Valency Cells

 


Carry Select Adder

 
- Trick for critical paths dependent on late input X
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- Carry-select adder precomputes n-bit sums for both possible carries into n-bit group




$$t_{\text{select}} = t_{pg} + [n + (k - 2)]t_{AO} + t_{\text{mux}}$$

Carry Increment Adder

 

 


(a)

 


(b)

FIGURE 11.26 Variable-length carry-increment adder

4 bit Conditional Sum

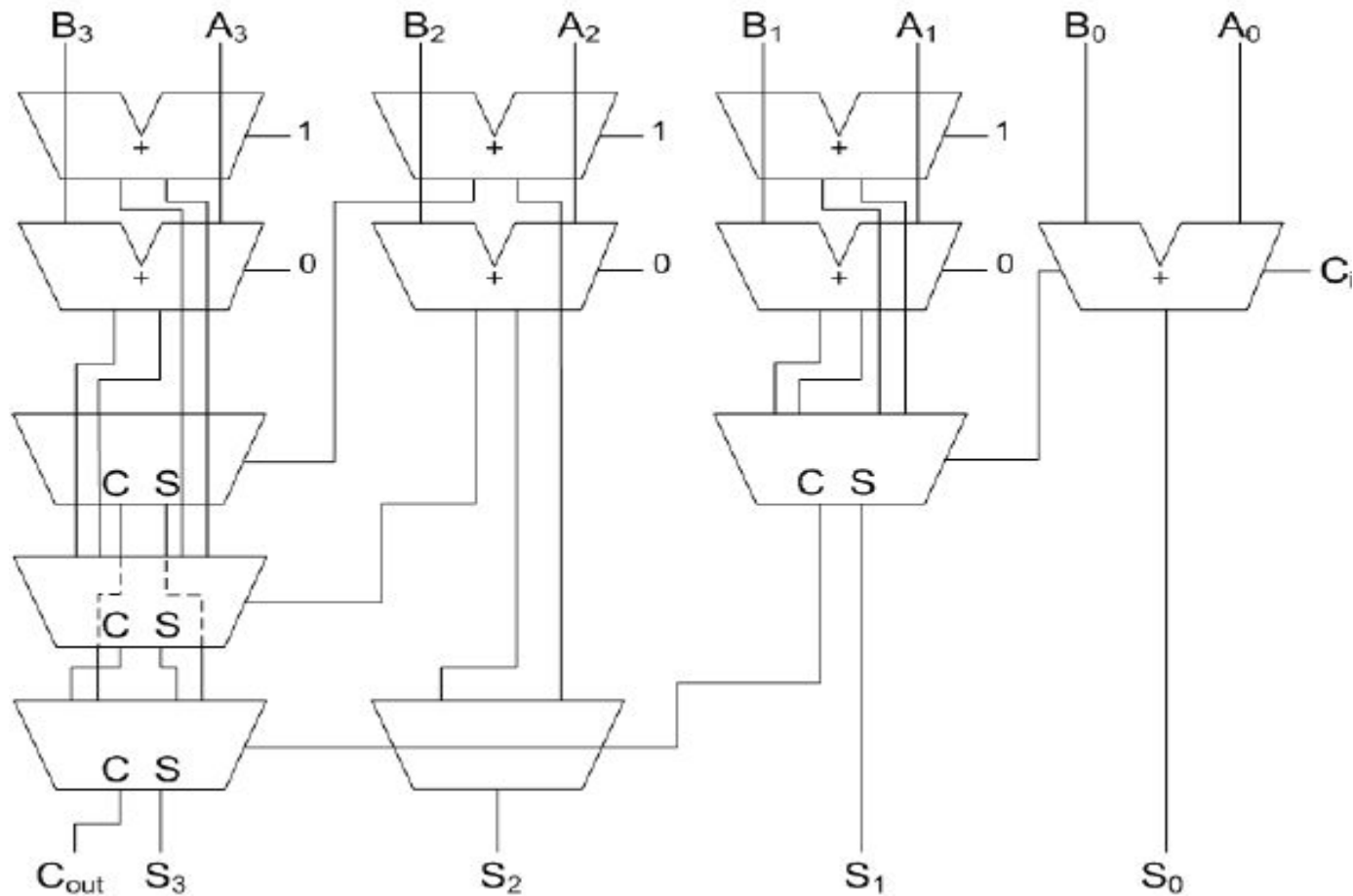

16 bit Conditional Sum Adder

 


16-Bit Conditional Sum Adder Example

		x	0	0	1	0	0	1	1	0	1	1	1	0	1	0	1	0	
		y	0	1	0	0	1	0	1	1	0	1	0	1	1	1	0	1	
Block width	Block carry-in	Block sum and block carry-out																	C _{in}
		15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0		
1	0	s	0	1	1	0	1	1	0	1	1	0	1	1	0	1	1	1	
	c	0	0	0	0	0	0	1	0	0	0	1	0	0	1	0	0	0	
1	1	s	1	0	0	1	0	0	1	0	0	1	0	0	1	0	0		
	c	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1		
2	0	s	0	1	1	0	1	1	0	1	0	0	1	1	0	1	1	1	
	c	0		0		0		1		1		0		1		0			
1	1	s	1	0	1	1	0	0	1	0	0	1	0	0	1	0			
	c	0		0		1		1		1		1		1		1			
4	0	s	0	1	1	0	0	0	0	1	0	0	1	1	0	1	1	1	
	c	0				1				1				1		1			
1	1	s	0	1	1	1	0	0	1	0	0	1	0	0					
	c	0				1				1			1						
8	0	s	0	1	1	1	0	0	0	1	0	1	0	0	0	1	1	1	
	c	0									1								
1	1	s	0	1	1	1	0	0	1	0									
	c	0																	
16	0	s	0	1	1	1	0	0	1	0	0	1	0	0	0	1	1	1	
	c	0																	
1	1	s																	
	c																		
			C _{out}																



C_{out}

One/Zero Detectors

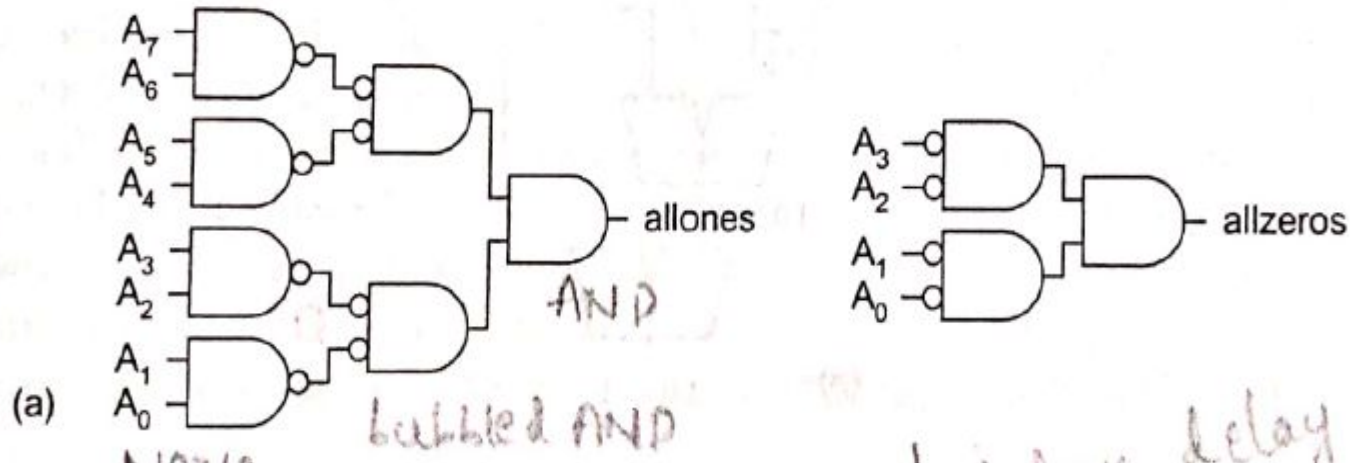


$$G_{\text{and}}(N) = \left(\frac{4}{3}\right)^{\log_2 N} = N^{\log_2 \frac{4}{3}} = N^{0.415}$$
 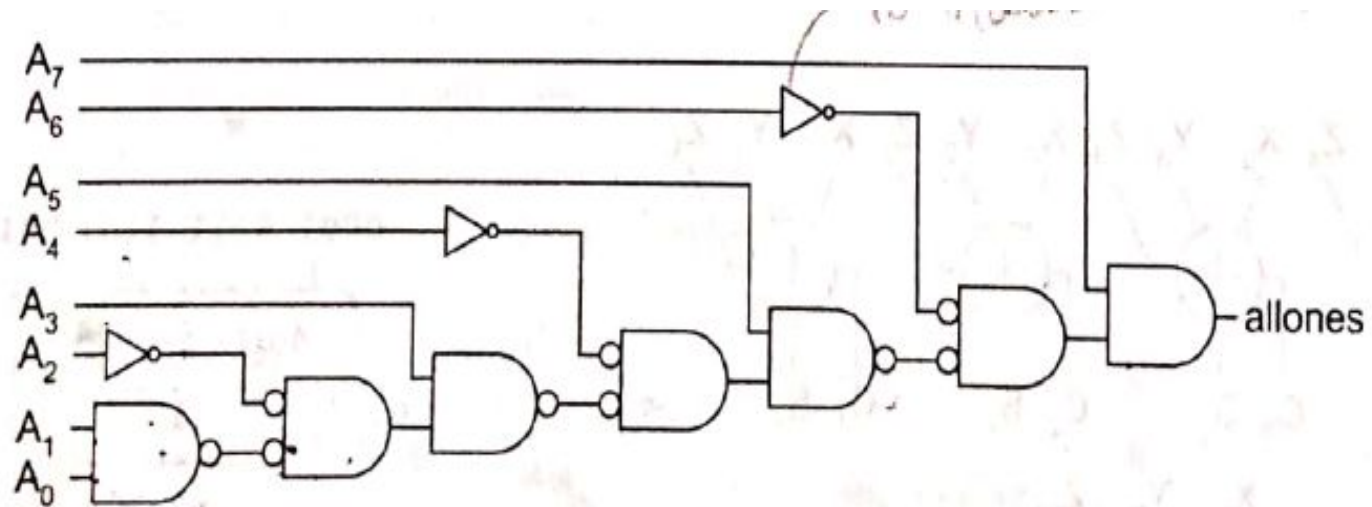
$$D \approx (\log_4 F) t_{FO4} = (\log_4 H + 0.415 \log_4 N) t_{FO4}$$



Magnitude Comparator

 - ❑ Compute $B-A$ and look at sign
- ❑ $B-A = B + \sim A + 1$
- ❑ For unsigned numbers, carry out is sign bit



Signed vs Unsigned


- ❑ For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)

Table 10.4 Magnitude comparison

Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\overline{Z}	\overline{Z}
$A < B$	$\overline{C} + Z$	$\overline{(N \oplus V)} + Z$
$A > B$	\overline{C}	$(N \oplus V)$
$A \leq B$	C	$(\overline{N \oplus V})$
$A \geq B$	$\overline{C} + Z$	$(N \oplus V) + Z$

Equality Comparator

 - ❑ Check if each bit is equal (XNOR, aka equality gate)
- ❑ 1's detect on bitwise equality



Shifters

❑ Logical Shift:

– Shifts number left or right and fills with 0's

• $1011 \text{ LSR } 1 = 0101$ $1011 \text{ LSL } 1 = 0110$

❑ Arithmetic Shift:

– Shifts number left or right. Rt shift sign extends

• $1011 \text{ ASR } 1 = 1101$ $1011 \text{ ASL } 1 = 0110$


❑ Rotate:

– Shifts number left or right and fills with lost bits

• $1011 \text{ ROR } 1 = 1101$ $1011 \text{ ROL } 1 = 0111$

Funnel Shifters

 - ❑ A funnel shifter can do all six types of shifts
- ❑ Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shift Operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N-k$
Rotate Right	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	$N-k$

❑ Computing $N-k$ requires an adder



Simplified Funnel Shifter

- Optimize down to $2N-1$ bit input

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1}...A_0$	k
Logical Left	$A_{N-1}...A_0, 0..0$	\bar{k}
Arithmetic Right	$A_{N-1}...A_{N-1}, A_{N-1}...A_0$	k
Arithmetic Left	$A_{N-1}...A_0, 0..0$	\bar{k}
Rotate Right	$A_{N-2}...A_0, A_{N-1}...A_0$	k
Rotate Left	$A_{N-1}...A_0, A_{N-1}...A_1$	\bar{k}


Funnel Shifter Design-1

  - ❑ N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (V_t drops!)




Funnel Shifter Design-2

 - Log N stages of 2-input muxes
 - No select decoding needed



Universal Shift Register

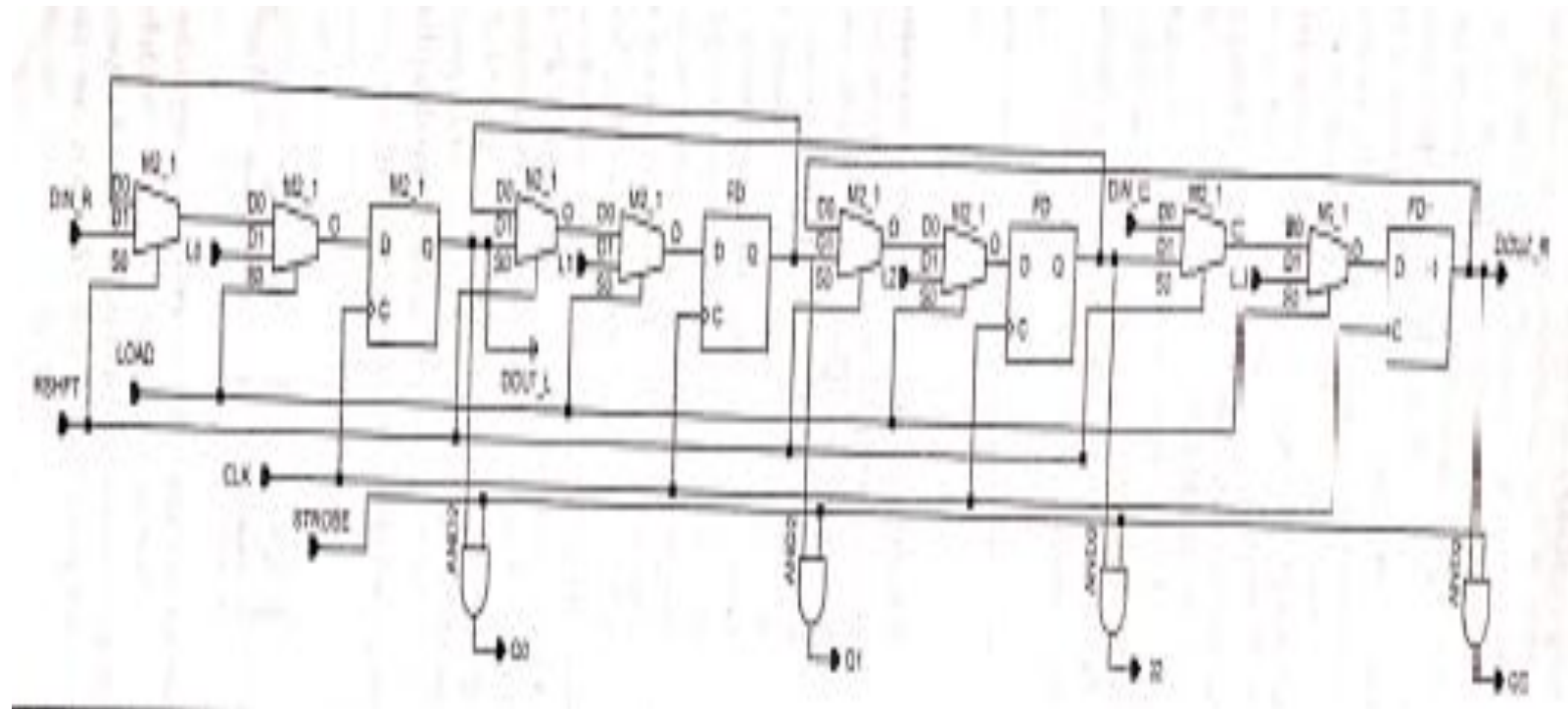

Multiplication

□ Example:

$$\begin{array}{rcl} 1100 & : & 12_{10} \\ \underline{0101} & : & 5_{10} \end{array}$$

Multiplication

□ Example:

1100	:	12_{10}	multiplicand
0101	:	5_{10}	multiplier
<hr/>			
1100			partial products
0000			
1100			
0000			
<hr/>			
00111100	:	60_{10}	product

□ M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

General Form

❑ Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$


❑ Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

❑ Product: $P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$

						y_5	y_4	y_3	y_2	y_1	y_0	multiplicand
						x_5	x_4	x_3	x_2	x_1	x_0	
						$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$	partial products
					$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$		
				$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$			
			$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$				
		$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$					
	$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$						
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	product

Dot Diagram

- ❑ Each dot represents a bit

 

Efficient Parallel Approaches

- Unsigned Multiplication
- 2's Complement
- Wallace trees
- Hybrid array/tree structures
- Serial Multiplications