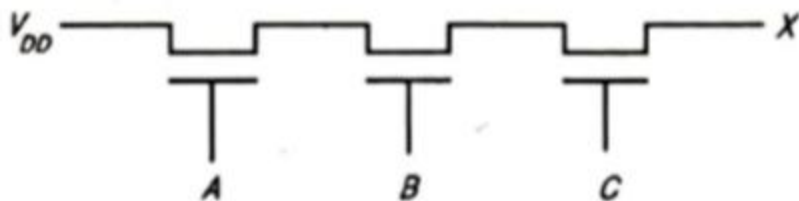


# The Pass Transistor



Pass transistor And gate.

$$\underline{X} = A.B.C \text{ (Logic 1 = } V_{DD} - V_t \text{)}$$

The output conductance  $g_{ds}$  can be expressed by

$$g_{ds} = \frac{\delta I_{ds}}{\delta V_{gs}} = \lambda \cdot I_{ds} \propto \left(\frac{1}{L}\right)^2$$

Here the strong dependence on the channel length is demonstrated as

$$\lambda \propto \left(\frac{1}{L}\right) \text{ and } I_{ds} \propto \left(\frac{1}{L}\right)$$

for the MOS device.

# The nMOS Inverter

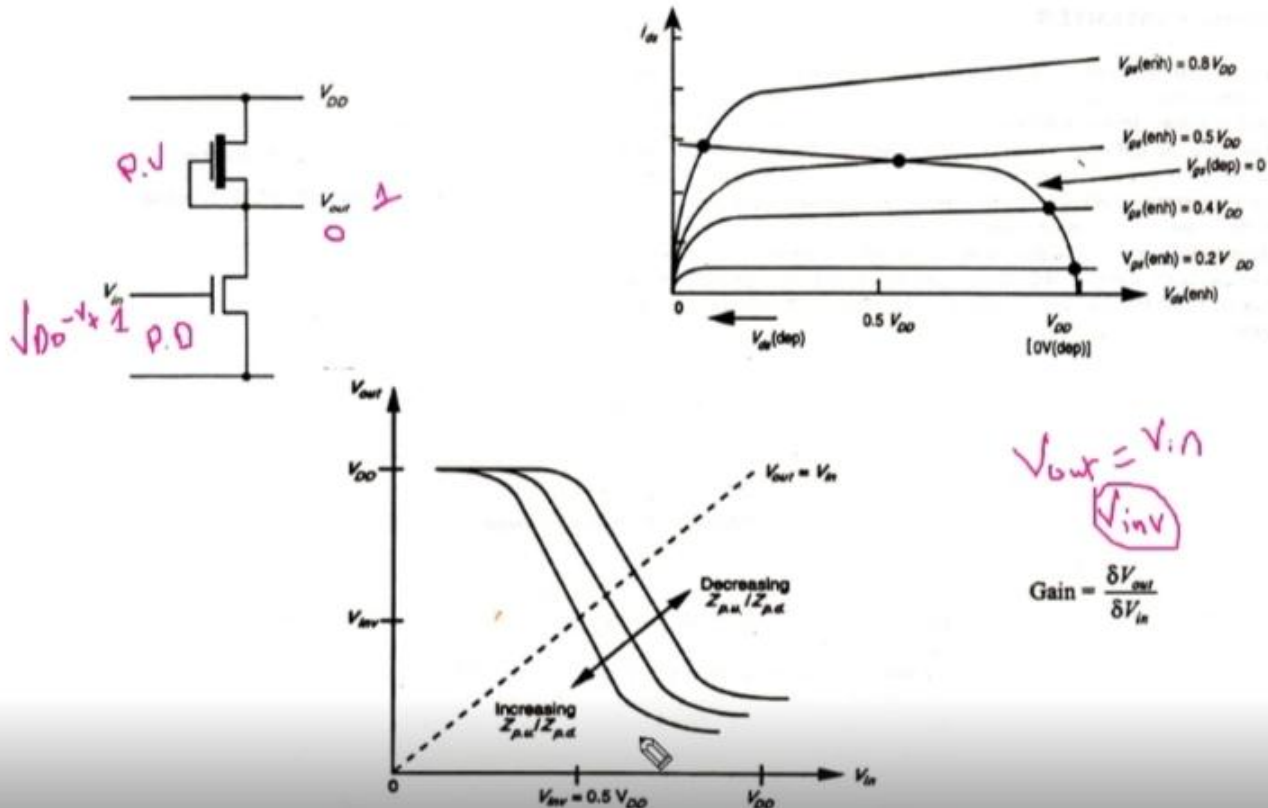


FIGURE 2.7 nMOS inverter transfer characteristic.

## DETERMINATION OF PULL-UP TO PULL-DOWN RATIO ( $Z_{p.u}\}$ $Z_{p.d.}$ ) FOR AN nMOS INVERTER DRIVEN BY ANOTHER nMOS INVERTER

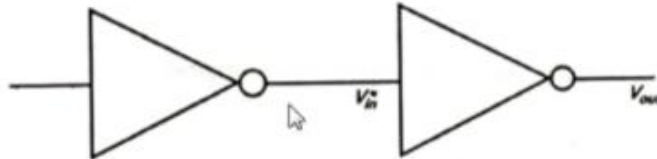


FIGURE 2.8 nMOS inverter driven directly by another inverter.

For equal margins around the inverter threshold, we set  $V_{inv} = 0.5 V_{DD}$ . At this point both transistors are in saturation and

$$I_{ds} = K \frac{W}{L} \frac{(V_{gs} - V_t)^2}{2}$$

In the depletion mode

$$I_{ds} = K \frac{W_{p.u}}{L_{p.u}} \frac{(-V_{td})^2}{2} \text{ since } V_{gs} = 0$$

and in the enhancement mode

$$I_{ds} = K \frac{W_{p.d.}}{L_{p.d.}} \frac{(V_{inv} - V_t)^2}{2} \text{ since } V_{gs} = V_{inv}$$

Equating (since currents are the same) we have

$$\frac{W_{p.d.}}{L_{p.d.}} (V_{inv} - V_t)^2 = \frac{W_{p.u.}}{L_{p.u.}} (-V_{td})^2$$

$$Z_{p.d.} = \frac{L_{p.d.}}{W_{p.d.}}; Z_{p.u.} = \frac{L_{p.u.}}{W_{p.u.}}$$

we have

$$\frac{1}{Z_{p.d.}} (V_{inv} - V_t)^2 = \frac{1}{Z_{p.u.}} (-V_{td})^2$$

whence

$$V_{inv} = V_t - \frac{V_{td}}{\sqrt{Z_{p.u.}/Z_{p.d.}}} \quad (2.9)$$

Now we can substitute typical values as follows:

$$V_t = 0.2V_{DD}; V_{td} = -0.6V_{DD}$$

$$V_{inv} = 0.5V_{DD} \text{ (for equal margins)}$$

thus, from equation (2.9)

$$0.5 = 0.2 + \frac{0.6}{\sqrt{Z_{p.u.}/Z_{p.d.}}}$$

## PULL-UP TO PULL-DOWN RATIO FOR AN nMOS INVERTER DRIVEN THROUGH ONE OR MORE PASS TRANSISTORS

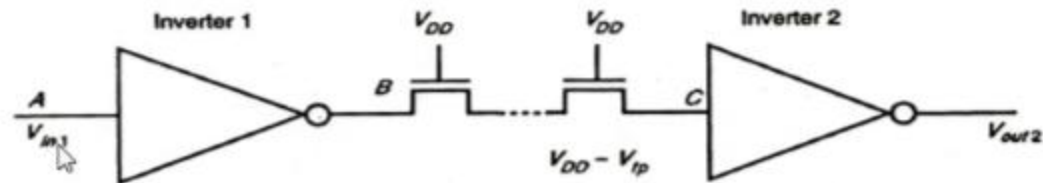


FIGURE 2.9 Pull-up to pull-down ratios for inverting logic coupled by pass transistors.

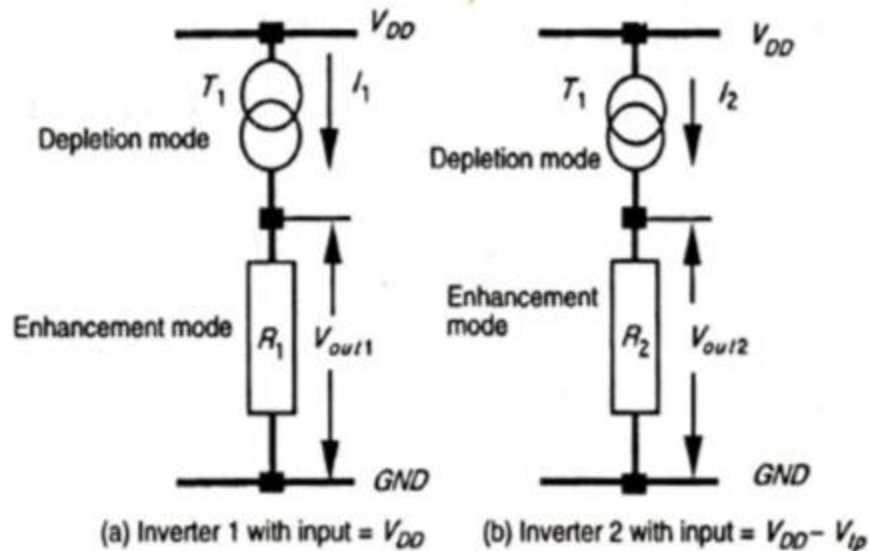


FIGURE 2.10 Equivalent circuits of inverters 1 and 2.

For the p.d. transistor

$$I_{ds} = K \frac{W_{p.d.1}}{L_{p.d.1}} \left( (V_{DD} - V_t) V_{ds1} - \frac{V_{ds1}^2}{2} \right) \quad (\text{from 2.4})$$

Therefore

$$R_1 = \frac{V_{ds1}}{I_{ds}} = \frac{1}{K} \frac{L_{p.d.1}}{W_{p.d.1}} \left( \frac{1}{V_{DD} - V_t - \frac{V_{ds1}}{2}} \right)$$

Note that  $V_{ds1}$  is small and  $V_{ds1}/2$  may be ignored.

Thus

$$R_1 \approx \frac{1}{K} Z_{p.d.1} \left( \frac{1}{V_{DD} - V_t} \right)$$

Now, for depletion mode p.u. in saturation with  $V_{gs} = 0$

$$I_1 = I_{ds} = K \frac{W_{p.u.1}}{L_{p.u.1}} \frac{(-V_{td})^2}{2}$$

(from 2.5)

The product

$$I_1 R_1 = V_{out1}$$

Thus

$$V_{out1} = I_1 R_1 = \frac{Z_{p.d.1}}{Z_{p.u.1}} \left( \frac{1}{V_{DD} - V_t} \right) \frac{(V_{td})^2}{2}$$

Consider inverter 2 (Figure 2.10(b)) when input =  $V_{DD} - V_{tp}$ . As for inverter 1

$$R_2 \approx \frac{1}{K} Z_{p.d.2} \frac{1}{((V_{DD} - V_{tp}) - V_t)}$$

$$\begin{aligned} & \frac{V_{ds1}}{K \frac{W_{p.d.1}}{L_{p.d.1}} \left( (V_{DD} - V_t) - \frac{V_{ds1}}{2} \right)} \approx V_{ds1} \\ & (V_{in} - V_t)^2 = \frac{Z_{p.d.1}}{Z_{p.u.1}} (-V_{td})^2 \\ & V_{in} - V_t = \frac{V_{td}}{\sqrt{Z_{p.d.1}/Z_{p.u.1}}} \end{aligned}$$

$$\begin{aligned} & K \frac{W_{p.u.1}}{L_{p.u.1}} \frac{(-V_{td})^2}{2} \times \frac{1}{K} \frac{Z_{p.d.1}}{Z_{p.u.1}} \frac{1}{(V_{DD} - V_t)} = \frac{1}{V_{DD} - V_t} \\ & \frac{Z_{p.d.1}}{Z_{p.u.1}} \frac{1}{(V_{DD} - V_t)} \left( \frac{V_{td}^2}{2} \right) \end{aligned}$$

$$I_2 = K \frac{1}{Z_{p,u,2}} \frac{(-V_{td})^2}{2}$$

whence

$$V_{out 2} = I_2 R_2 = \frac{Z_{p,d,2}}{Z_{p,u,2}} \left( \frac{1}{V_{DD} - V_{tp} - V_t} \right) \frac{(-V_{td})^2}{2}$$

If inverter 2 is to have the same output voltage under these conditions then  $V_{out 1} = V_{out 2}$ .  
That is

$$I_1 R_1 = I_2 R_2$$

Therefore

$$\frac{Z_{p,u,2}}{Z_{p,d,2}} = \frac{Z_{p,u,1}}{Z_{p,d,1}} \frac{(V_{DD} - V_t)}{(V_{DD} - V_{tp} - V_t)}$$

Taking typical values

$$V_t = 0.2V_{DD}$$

$$V_{tp} = 0.3V_{DD}^*$$

$$\frac{Z_{p,u,2}}{Z_{p,d,2}} = \frac{Z_{p,u,1}}{Z_{p,d,1}} \frac{0.8}{0.5}$$

Therefore

$$\frac{Z_{p,u,2}}{Z_{p,d,2}} = 2 \frac{Z_{p,u,1}}{Z_{p,d,1}} = \frac{8}{1}$$

$$\frac{Z_{p,d,1}}{Z_{p,u,1}} \left( \frac{1}{V_{DD} - V_{tp}} \right) \frac{(V_{DD} - V_t)^2}{2} =$$

$$\frac{Z_{p,d,2}}{Z_{p,u,2}} \left( \frac{1}{V_{DD} - V_{tp} - V_t} \right) \frac{(V_{DD} - V_t)^2}{2}$$