

Inverter Switching Characteristics



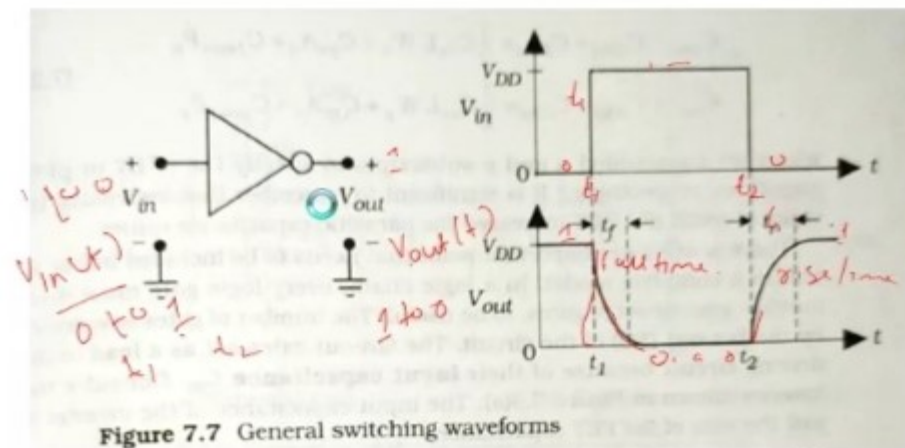



Figure 7.7 General switching waveforms

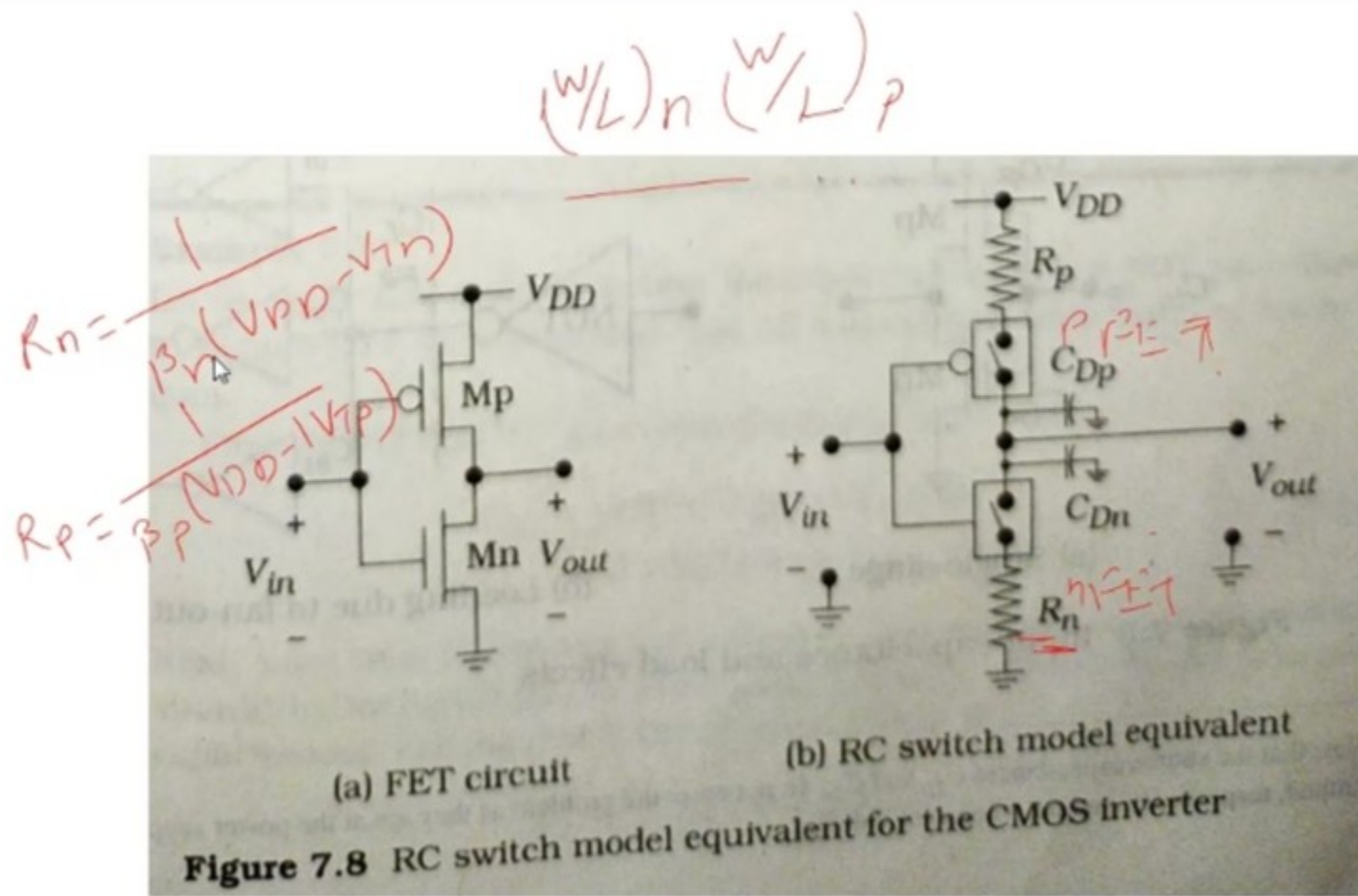

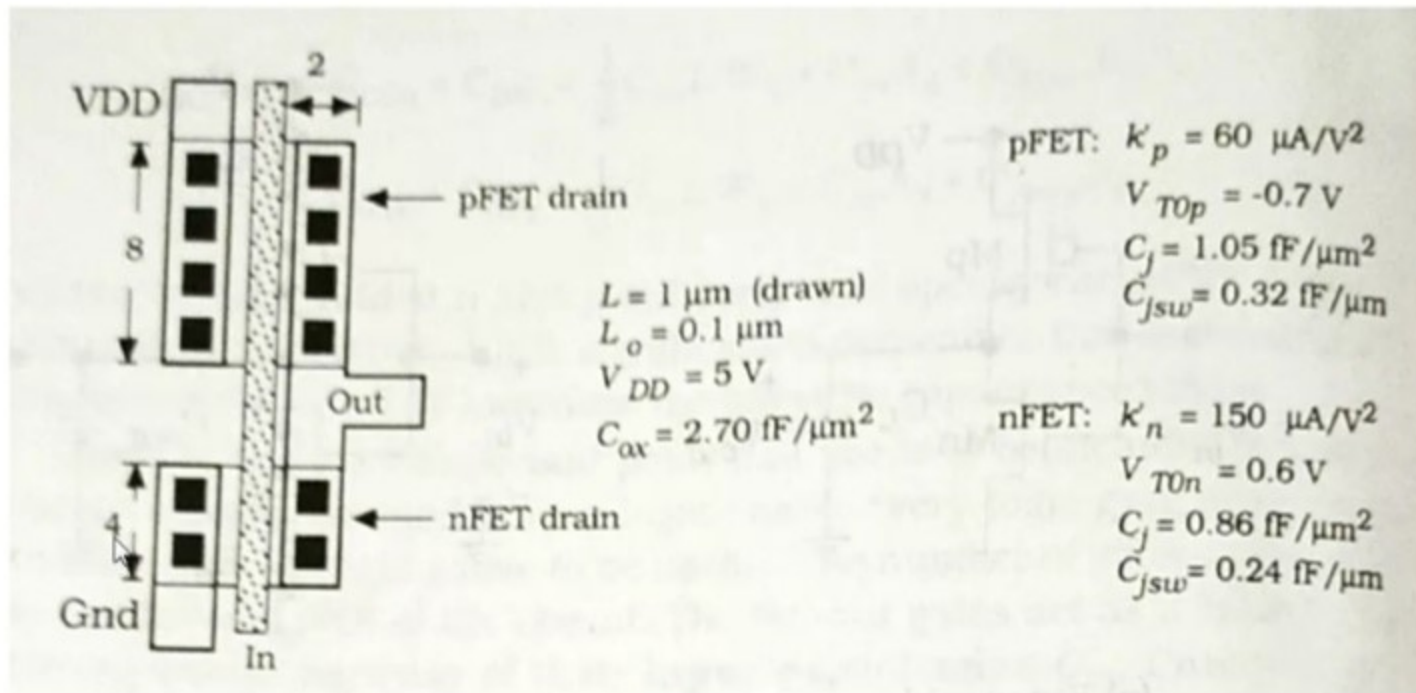Example: Analysis to Find the Capacitances in the NOT gate



Fall Time Calculation

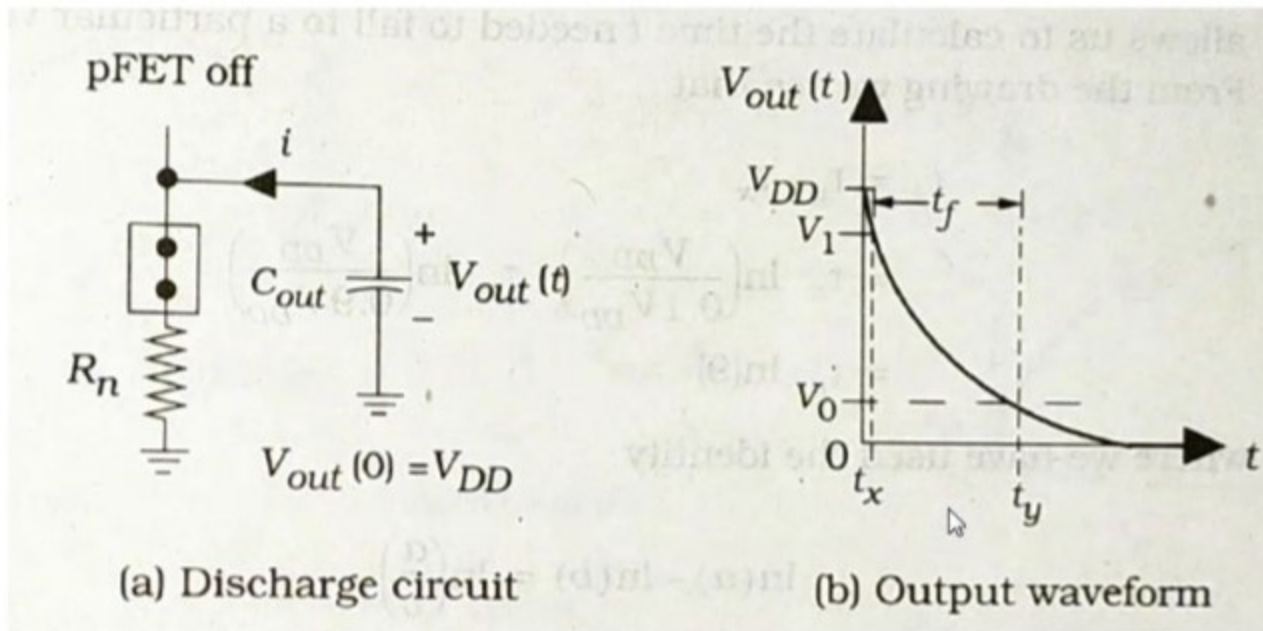

$$i = -C_{out} \frac{dV_{out}}{dt} = \frac{V_{out}}{R_n}$$

$$\frac{dV_{out}}{dt} = x$$

$$-C_{out} x = \frac{V_{out}}{R_n}$$

$$-C_{out} R_n x = V_{out}$$

$$x = -\frac{V_{out}}{R_n C_{out}}$$

$$x = -\frac{V_{out}}{\tau_n}$$

$$V_{out}(t) = V_{out}(0) e^{-t/\tau_n}$$

$$t_x = \tau_n \ln\left(\frac{V_{0.1}}{V_{0.9}}\right)$$

$$t = 2.2 \tau_n$$

$$V_{out}(0) = V_{DD}$$

$$V_{out}(t) = V_{DD} e^{-t/\tau_n}$$

$$\tau_n = R_n C_{out}$$

$$e^{-t/\tau_n} = \frac{V_{out}(t)}{V_{DD}}$$

$$-\frac{t}{\tau_n} = \ln\left(\frac{V_{out}(t)}{V_{DD}}\right)$$

$$t = -\tau_n \ln\left(\frac{V_{out}(t)}{V_{DD}}\right)$$

$$= \tau_n \ln\left(\frac{V_{DD}}{V_{out}(t)}\right)$$

$$0.1 V_{DD} \quad 0.9 V_{DD}$$

$$t_f = t_y - t_x$$

$$= \tau_n \ln\left(\frac{V_{DD}}{0.1 V_{DD}}\right) - \tau_n \ln\left(\frac{V_{DD}}{0.9 V_{DD}}\right)$$

meet.google.com is sharing your screen.

Stop sharing

Hide

$$C_{FE_T} = C_{on} + C_{op} = 15.552 + 34.9 = 50.45 \text{ fF}$$

$$C_{out} = C_{FE_T} + C_L$$

$$C_{out} = 50.45 \text{ fF} + C_L$$