

## 2. nMOS depletion mode transistor pull-up



 


FIGURE 2.12 nMOS depletion mode transistor pull-up and transfer characteristic.
 
#### 4. Complementary transistor pull up PMOS




(a) Circuit

 

(b) Transfer characteristic

# Alternative forms of Pull-Up


## 1. Load resistance $R_L$

 

# DC Characteristics of the CMOS Inverter

## 1. DC Analysis

## 2. Transient Analysis

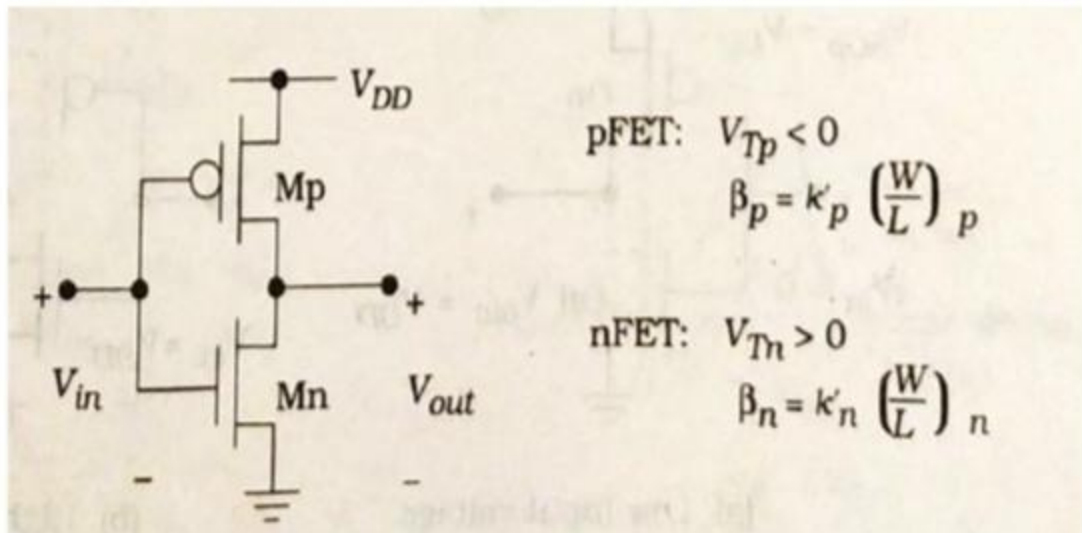


# Voltage Transfer Characteristics

$$V_{OH} = V_{DD}$$

$$V_{OL} = 0V$$

$$V_L = V_{OH} - V_{OL} = V_{DD}$$

$$V_{in} = 0V$$

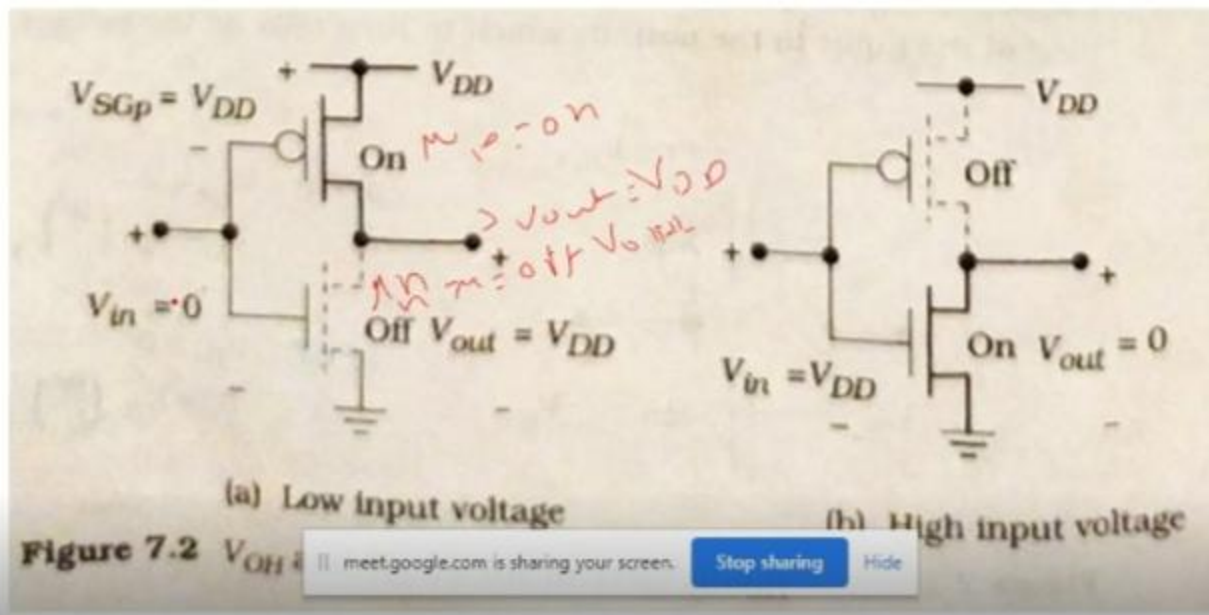

The VTC for the circuit is obtained by starting with an input voltage of  $V_{in}=0$  and then increasing it up to the value of  $V_{in}=V_{DD}$

$$V_{Gsn}=V_{in}$$

$$V_{Gsp}=V_{DD}-V_{in}$$

$$V_{in} = V_{DD} - |V_{Tp}|$$

$$0 < V_{in} < \frac{V_{DD}}{2}$$


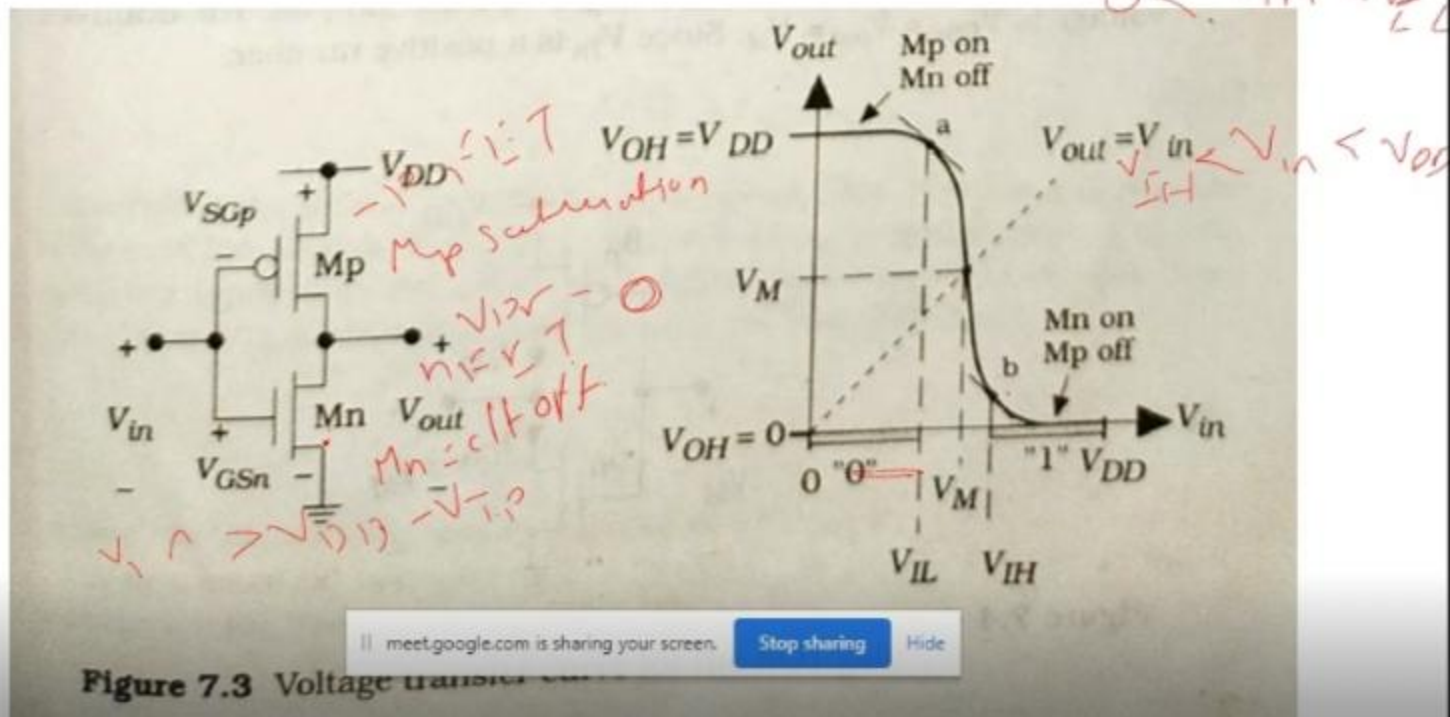


Figure 7.3 Voltage transfer characteristics (VTC) of an inverter.

## Inverter Voltages for VM calculations

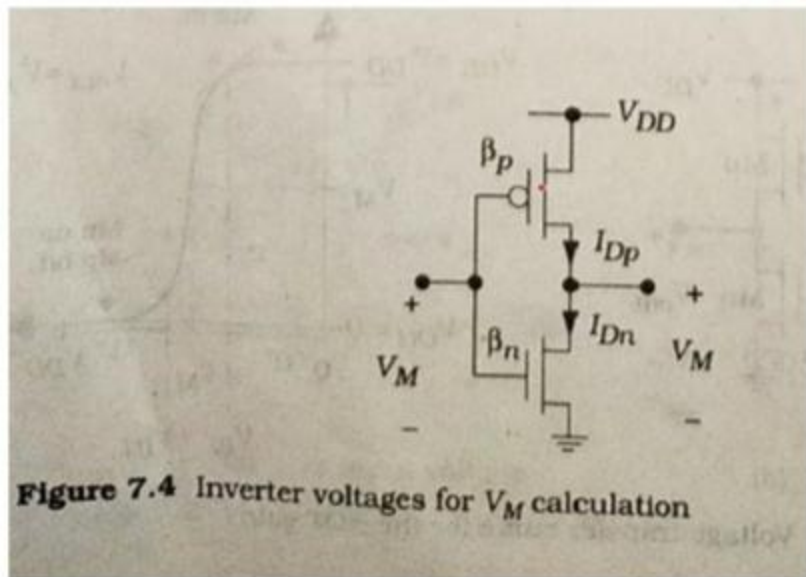

**Figure 7.4** Inverter voltages for  $V_M$  calculation

$$V_M - V_{th} = V_{in}$$

$$I_{Dp} = I_{Dn}$$

To calculate the midpoint voltage we set  $V_{in} = V_{out} = V_M$  as shown in Figure 7.4. Equating the drain currents of the FETs gives

$$I_{Dn} = I_{Dp} \quad (7.9)$$

but we need to find the operating region (saturation or non-saturation) of each FET before we can use the expression. Consider first the nFET and recall that the saturation voltage is given by

$$\begin{aligned} V_{sat} &= V_{GSn} - V_{Tn} \\ &= V_M - V_{Tn} \end{aligned} \quad (7.10)$$

where we have used  $V_{in} = V_{GSn} = V_M$  in the second line. The drain-source voltage is  $V_{DSn} = V_{out} = V_M$ . Since  $V_{Tn}$  is a positive number,

$$V_{DSn} > V_{sat} = V_M - V_{Tn} \quad (7.11)$$

which says that Mn must be saturated. The same arguments can be applied to the pFET Mp since  $V_{SGp} = V_{SDp}$ . Using the saturation current equations from Chapter 6 gives

$$\frac{\beta_n}{2}(V_M - V_{Tn})^2 = \frac{\beta_p}{2}(V_{DD} - V_M - |V_{Tp}|)^2 \quad (7.12)$$



Dividing by  $\beta_p$  and taking the square root gives

$$\sqrt{\frac{\beta_n}{\beta_p}}(V_M - V_{Tn}) = V_{DD} - V_M - |V_{Tp}|$$

$$\sqrt{\frac{\beta_n}{\beta_p}} V_M - \sqrt{\frac{\beta_n}{\beta_p}} V_{Tn} = V_{DD} - V_M - |V_{Tp}| \quad (7.13)$$

Simple algebra then gives the midpoint voltage as

$$V_M = \frac{V_{DD} - |V_{Tp}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{Tn}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

$$\sqrt{\frac{\beta_n}{\beta_p}} V_M + V_M = V_{DD} - |V_{Tp}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{Tn} \quad (7.14)$$

$$V_M \left( \sqrt{\frac{\beta_n}{\beta_p}} + 1 \right) = V_{DD} - |V_{Tp}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{Tn}$$

This equation shows that  $V_M$  is set by the nFET-to-pFET ratio

$$\frac{\beta_n}{\beta_p} = \frac{k'_n \left( \frac{W}{L} \right)_n}{k'_p \left( \frac{W}{L} \right)_p} \quad (7.15)$$

$$\frac{k'_n}{k'_p} = 2 \text{ to } 3 \quad (7.16)$$

$$\frac{k'_n}{k'_p} = \frac{\mu_n}{\mu_p} = r \quad (7.17)$$

$$V_M = \frac{1}{2} V_{DD} \quad (7.18)$$

in equation (7.12). Rearranging gives us the design equation

$$\frac{\beta_n}{\beta_p} = \left( \frac{\frac{1}{2} V_{DD} - |V_{Tp}|}{\frac{1}{2} V_{DD} - V_{Tn}} \right)^2 \quad (7.19)$$

This allows us to compute the transistor sizes for this particular choice of  $V_M$ . Note that if  $V_{Tn} = |V_{Tp}|$ , then a symmetric design requires that

$$\beta_n = \beta_p \quad (7.20)$$