
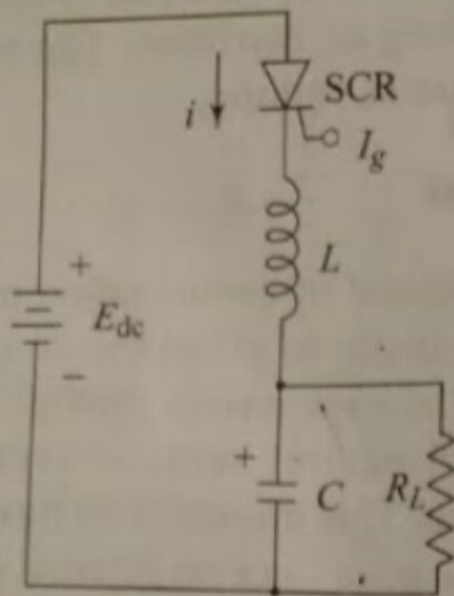


pmysurNagaraj

Fig. 3.2: Simplified model of a thyristor

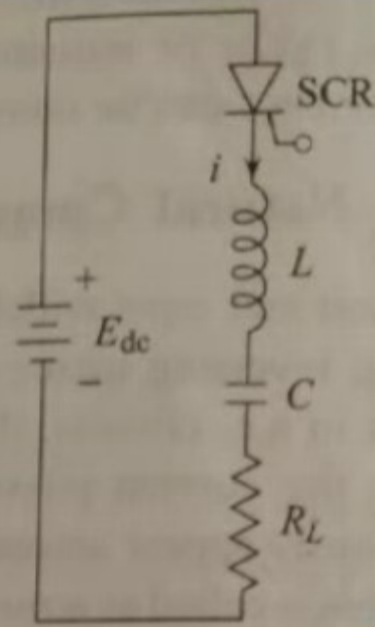


(a) Load in parallel with capacitor




(b) Load in series with capacitor


Fig. 2.12 Class A commutation circuit

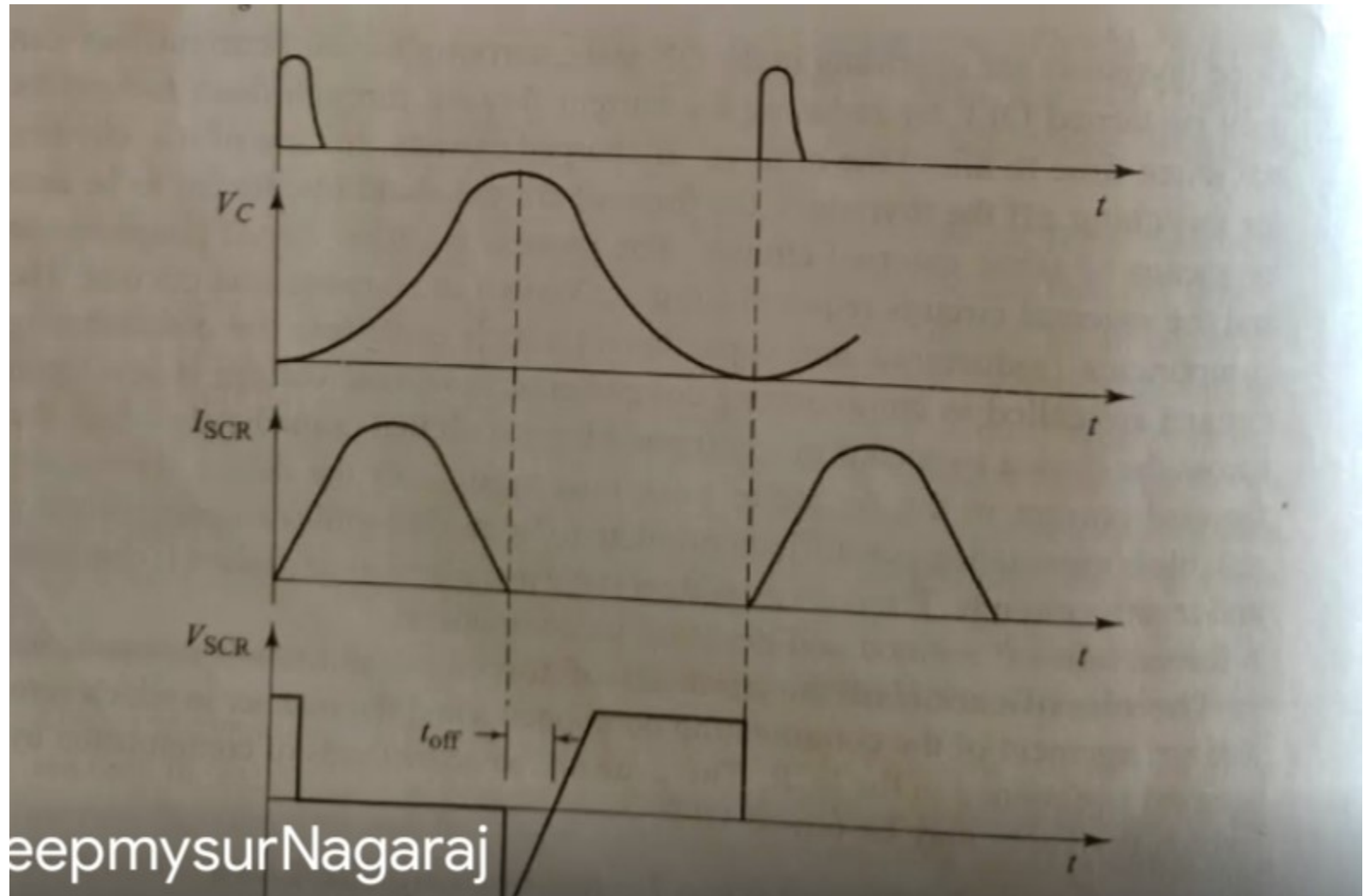

deepmysurNagaraj

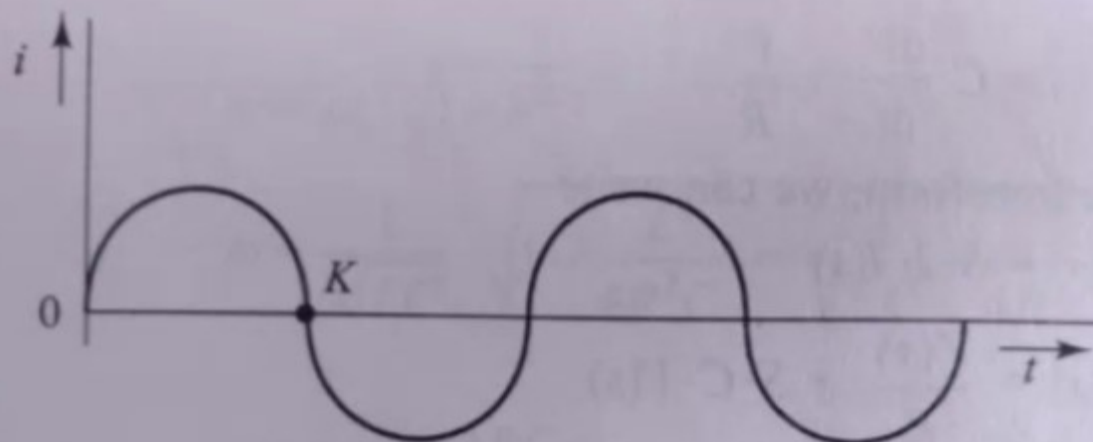

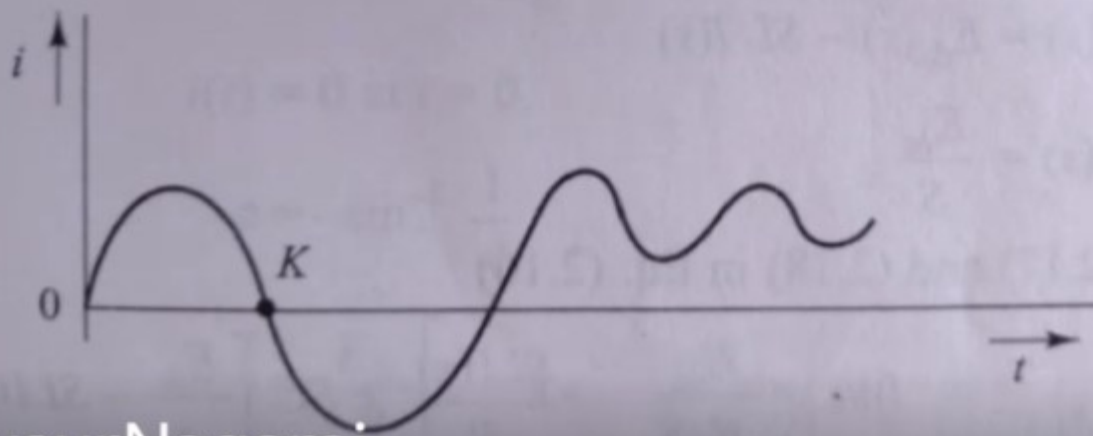(a) Waveforms of the current produced in Fig. 2.12(b) (series capacitor)



pmysurNagaraj

(b) waveforms of the current produced in Fig. 2.12(a) (parallel capacitor)