

FIGURE 3.2 Stick diagrams and corresponding mask layout examples.

## Generalized AOI and OAI Logic Gates


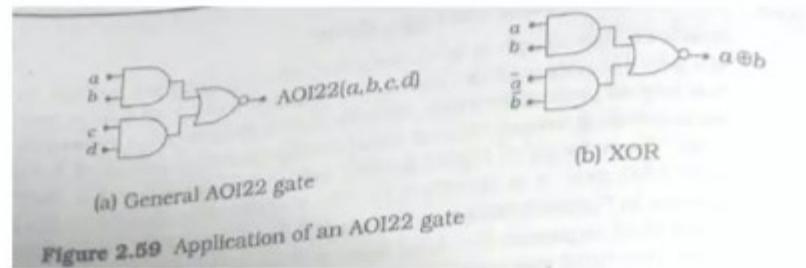


Figure 2.59 Application of an AOI22 gate

# Transmission Gate Circuits

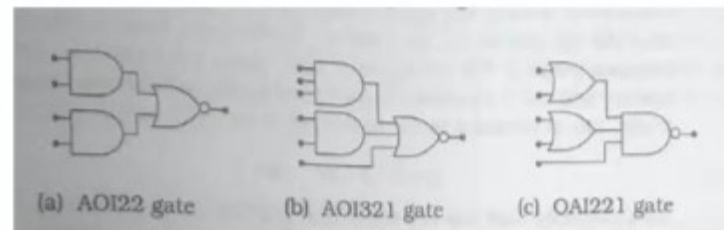